

2015

ELECTRONICS

[ Honours ]

PAPER – III (Theory)

Full Marks : 100

Time : 4 hours

*The figures in the right hand margin indicate marks  
Candidates are required to give their answers in their  
own words as far as practicable*

*Illustrate the answers wherever necessary*

GROUP – A

Answer any two questions :  $15 \times 2$ 

1. (a) Determine the current through the load  $R_L$  of the following circuit using Kirchhoff's current Law.

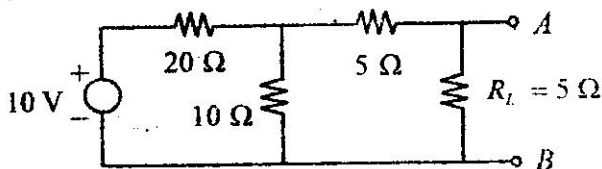


Fig. 1

( Turn Over )

(b) What do you mean by the 'node' and branch of a Network ?

(c) Derive the expression of loop current  $i(t)$  of the following circuit for  $t > 0$ . The 'K' switch closes the circuit at  $t = 0$ .

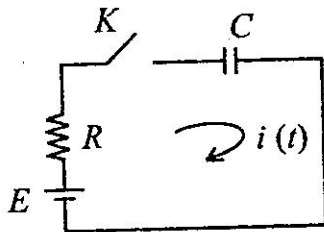


Fig. 2

Also determine the steady state value of  $i(t)$ .

(d) Write down the principle of operation of a Wien bridge. 5 + 2 + (4 + 1) + 3

2. (a) Discuss the terms of depletion capacitance and diffusion capacitance in connection with a P-N junction diode.

- (b) Explain with a neat circuit diagram how a Zener diode can be used as a voltage regulator.
- (c) A transistor amplifier in *CE* configuration couples a source of internal resistance  $1\text{ K}\Omega$  to a load of  $20\text{ K}\Omega$ . Find the input and the output resistances if  $h_{ie} = 1\text{ K}\Omega$ ,  $h_{re} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 150$  and  $1/h_{oe} = 40\text{ K}\Omega$ .
- (d) Explain the principle of operation of a CMOS inverter with suitable circuit diagram. 2 + 4 + 5 + 4
3. (a) What are the fundamental differences among the class A, class B and class C amplifiers ?
- (b) Draw the circuit diagram of a two-stage *RC* coupled *CE* transistor amplifiers. Show how the magnitude and phase angle of its voltage gain vary with frequency. Qualitatively explain these variations. Define half power frequencies.

- (c) Explain with a circuit diagram the operation of a single tuned amplifier. Draw its ac equivalent circuit and find an expression for the voltage gain and bandwidth.


$$3 + (2 + 2 + 2) + (2 + 4)$$

### GROUP – B

Answer any **five** questions : 8 × 5

4. (a) The arm impedance of a  $\pi$  network are  $Z_A = 20 \Omega$ ,  $Z_B = j 30 \Omega$  and  $Z_C = 40 \Omega$ . Calculate the arm impedance of an equivalent  $T$  network.
- (b) With a neat sketch discuss the principle of operation of a transformer. 5 + 3
5. (a) What is the difference between an enhancement type and a depletion type MOSFET?
- (b) Deduce the relationship  $\mu = r_d \cdot g_m$  for a field effect transistor.
- (c) Derive the expression of pinch-off voltage of a field effect transistor. 2 + 3 + 3

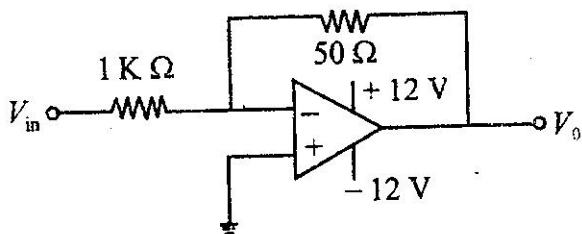6. (a) Compute the output voltage  $V_o$  of the following circuit when input is  $V_{in} = 0.5 \sin 100 \pi t$ :



- (b) Discuss how an OPAMP can be used as a differentiator? 5 + 3
7. (a) What is an emitter follower? Discuss the principle of operation of a Darlington Amplifier.
- (b) Using  $h$ -parameter model of a transistor derive the expressions of input resistance and current gain. (2 + 2) + (2 + 2)
8. (a) State and prove the maximum power transfer theorem.
- (b) Indicate some application of thermocouples. 6 + 2

9. (a) With a neat circuit diagram discuss the principle of operation of a CMOS NAND gate.
- (b) Why MOS logic is preferred in IC fabrication in comparison with TTL logic ?  $6 + 2$
10. (a) Draw the energy band diagram of a photodiode and explain its operation. What is P-i-N photodiode ?
- (b) Discuss how avalanche photodiode works ?  $(3 + 2) + 3$
11. (a) Discuss the working principle of a push-pull amplifier.
- (b) Discuss how negative resistance is achieved in a GUNN diode ?  $5 + 3$

GROUP – C

Answer any **five** questions :  $4 \times 5$

12. Derive an expression of small-signal voltage gain of a common source FET amplifier.  $4$
13. Write a short note on Unijunction transistor.  $4$

14. What is a light emitting diode ? Why *silicon* is not preferred for LED material ? 2 + 2
15. Discuss the working principle of a phase-shift oscillator. 4
16. For a metal semiconductor contact prove that
- $$q\phi_{bn} + q\phi_{bp} = E_g. \quad 4$$
17. What do you mean by switched mode power supply ? Indicate some of its uses. 2 + 2
18. Explain the working principle of a Schmitt trigger using an OPAMP. 4
19. Explain the terms % regulation and ripple factors of a rectifier circuits. 2 + 2

[ *Internal Assessment* : 10 Marks ]

---