

2019

MSc

2nd Semester Examination

ELECTRONICS

PAPER – ELC-205(Prac.)

Full Marks: 50

Time: 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

PRACTICAL

ANSWER ANY **ONE** QUESTION SELECTING IT BY A LUCKY DRAW.

1. Design an astable multivibration using 555 timer for two different duty cycles. Duty cycles & frequency are to be provided at examination hall.
2. Design a four bit R -2R ladder network to convert a digital signal into analog signal.
3. Design a MOD – 13 ripple counter.
4. Design a random counter which will count the following states (1, 5, 7, 3, 2, 0, 4, 6)
5. Design a full adder circuit by NAND gates only.
Also realize the circuit by using 4:1 MUX.
6. Design J K & MS flip – flop convert then into T & D type flip – flops.
7. Design a MOD – 10 synchronous counter and show its counting states.
8. Design a full subtractor circuit by NAND gates only.
Also realize the circuit by using 4:1 MUX.
9. Design two bit comparator circuit.
Compare two binary numbers.

Distribution of marks

| | |
|---------------------------------|-------------|
| Theory | : 10 |
| Circuit (Implementation) | : 10 |
| Experiment | : 10 |
| Result and Discussion | : 10 |
| Viva – voce | : 10 |
| Lab note book | |
| | <hr/> |
| Total | 50 |