

M.Sc. 2nd Semester Examination, 2010

ELECTRONICS

(Digital Electronics)

(Theory)

PAPER —EL-1202

Full Marks : 40

Time : 2 hours

Answer Q.No.1 and any three questions from the rest.

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

1. Answer any five questions : 2 x 5

(a) Define Fan-in and Fan-out of a logic gate.

(b) One n -bit binary number is given, how do you determine that this number is divisible by 4 without doing any arithmetic ?

(Turn Over)

- (c) Explain how a Latch differs from a flip-flop.
- (d) Write down the principle of operation of a weighted register type D/A converter.
- (e) From the truth table of a T F/F prove that $Q(\epsilon+1) = T \bar{Q}(\epsilon) + \bar{T} Q(\epsilon)$.
- (f) Why a NAND gate is faster than an AND gate having same number of inputs ?

2. (a) Realise the cost effective circuit for the function $F = \Sigma m(2, 3, 5, 7, 10, 11, 13, 14, 15)$ using fundamental gates.

(b) Reduce the following Boolean expression

$$f = \bar{x} \bar{y} z + yz + z.$$


(c) What do mean by the dual of a digital circuit? 6+2+2

3. (a) What is a demultiplexer? How does it differ from a decoder? Implement the function

$$f = \bar{A} \bar{B} \bar{C} + A \bar{B} C + AB$$

using 3 to 8 decoder having active low outputs.

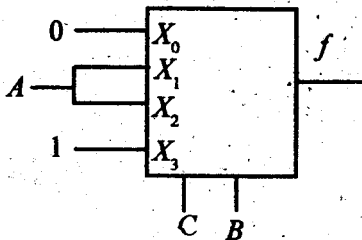- (b) A 4 to 1 multiplexer is connected with three logic inputs A , B , C as shown in the following figure. Find out the logical expression of f . (1 + 1 + 4) + 4



4. (a) What is function of clear ($\overline{\text{CLR}}$) and preset ($\overline{\text{PRE}}$) inputs of a flip-flop? Are they synchronous or asynchronous? (2 + 1) + 7
- (b) Design a counting circuit using all JK flip-flops to count an event up to ten and resets to 0 and recycles again.
5. (a) Briefly explain the operation of a $R-2R$ Ladder D/A converter and derive the expression of analog output voltage.

(b) A 10 bit resistive divider is constructed such that the current through the LSB resistor is $100 \mu\text{A}$. What will be the maximum current that will flow through the MSB resistor? $(3 + 4) + 3$

6. (a) What is a seven-segment display? How do you represent 7.01 using four seven-segment display?

(b) Design a BCD to excess-3 code converter using fundamental gates.

(c) Write short note on EPROM. $(1 + 2) + 5 + 2$