

M.Sc.**2011****4th Semester Examination****ELECTRONICS****PAPER—EL-2211****(PRACTICAL)**

Full Marks : 50

Time : 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

Answer any one question from either
PSPICE or Digital Electronics.

(PSPICE)

In each of the following questions, you have to save the design file by "your roll no., -design" and then save the plot in a file "your roll no. -plot".

1. Design an inverting amplifier circuit using PSPICE taking input resistor $R_1 = 1\text{k}\Omega$, feedback resistor $R_2 = 6.8\text{k}\Omega$ and load resistor $R_3 = 10\text{k}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit and plot the input


(Turn Over)

voltage V_{in} versus time and output voltage V_o versus time in same graph. Also verify the gain of the amplifier with its theoretical value.


2. Design a second order low pass Butterworth active filter with cut-off frequency 1KHZ in PSPICE. Simulate the circuit and plot the gain versus frequency curve. Also verify the cut-off frequency with its given value.
3. Design an astable multivibrator with frequency 1KHZ and duty cycle 66.67% using IC 555 in PSPICE. Simulate the circuit and plot the amplitude versus time curve. Also verify the frequency and duty cycle with its given value.
4. Create a PSPICE model of the non-inverting amplifier taking input resistor $R_1 = 1k\Omega$, feedback resistor $R_2 = 4.7 k\Omega$, and load resistor $R_3 = 10k\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit and plot the input voltage V_{in} versus time and output voltage V_o versus time in the same graph. Also verify the gain of the amplifier with its theoretical value.
5. Design a second order high pass Butterworth active filter with cut-off frequency 3KHZ in PSPICE. Simulate the circuit and plot the gain versus frequency curve. Also verify the cut-off frequency with its given value.
6. Design an inverting amplifier circuit using PSPICE taking input resistor $R_1 = 1k\Omega$, feedback resistor $R_2 = 10k\Omega$ and load resistor $R_3 = 10k\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit and plot the input

voltage V_{in} versus time and output voltage V_o versus time in same graph. Also verify the gain of the amplifier with its theoretical value.

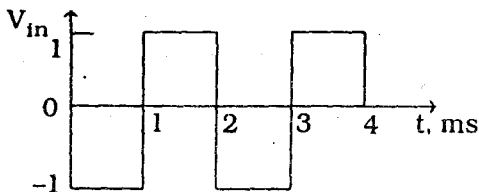7. Design an integrator circuit using op-amp taking input resistor $R_1 = 2.5k\Omega$, feedback resistor $R_2 = 1M\Omega$, feedback capacitor $C_2 = 0.1 \mu F$ and load resistor $R_3 = 100k\Omega$. Simulate the circuit using PSPICE and plot the transient response of the output voltage for a duration of 0 to 4 ms in steps of $50 \mu s$ for the input voltage given below.



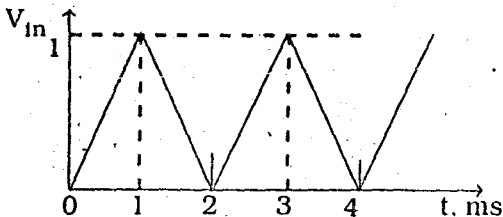8. Design a differentiator circuit using op-amp taking input Resistor $R_1 = 100\Omega$, input capacitor $C_1 = 0.4\mu F$, feedback resistor $R_2 = 10k\Omega$ and load resistor $R_3 = 100k\Omega$. Simulate the circuit using PSPICE and plot the transient response of the output voltage for a duration of 0 to 4 ms in steps of $10\mu s$ for the input voltage given below.



9. Design an astable multivibrator with frequency 10 KHZ and duty cycle 75% using 555IC. Simulate the circuit using PSPICE and plot the amplitude vs. time curve. Also verify the frequency and duty cycle with its given value.

Marks Distribution (For PSPICE)

- Theory — 07
 Circuit Design — 10
 Simulation — 10
 Verification and Accuracy — 05
 Discussion — 03
 Viva — 10
 Laboratory Note Book — 05

(Digital Electronics)

10. Design a 3-bit synchronous even counter using JK flip-flop. Verify the count sequence by LED display.
11. Design a 3-bit synchronous odd counter using JK flip-flops. Verify the count sequence by LED display.
12. Design a mod-5 synchronous down counter using JK FFs. Verify the count sequence by LED display.

Marks Distribution (For Digital)

- Theory — 05
 Circuit Design — 15
 Implementation — 07
 Experimental Result — 05
 Discussion — 03
 Viva — 10
 Laboratory Note Book — 05
-