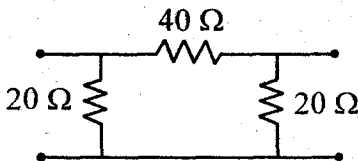


M.Sc. 1st Semester Examination, 2012**ELECTRONICS***(Network Analysis and Synthesis)**(Theory)*

PAPER—ELC-103

*Full Marks : 50**Time : 2 hours*Answer **Q. No. 1** and **three** questions from the rest*The figures in the right-hand margin indicate marks**Candidates are required to give their answers in their own words as far as practicable**Illustrate the answers wherever necessary*

1. (a) Define 'characteristic impedance' of a two port network.
- (b) Draw the equivalent *T*-section network for the given Π -section network.

*(Turn Over)*

- (c) Draw equivalent *CE*-transistor circuit using 'h'-parameters.
- (d) Test whether the following system function is positive real function or not

$$H(s) = \frac{s^2 + 10s + 5}{s + 3}$$

- (e) A network is expressed by the following differential equation :

$$5 \frac{d^2 y}{dt^2} + 3 \frac{dy}{dt} + 2y = 2 \frac{dx}{dt} + x$$


where, 'x' is the input and 'y' is the output obtain the transfer function. 2 × 5

2. (a) The reduced incidence matrix of a network is given below :

		Branches →					
		1	2	3	4	5	6
Nodes ↑	a	1	0	0	-1	0	0
	b	0	1	0	1	-1	0
	c	0	0	1	0	1	-1
	d	-----	-----	-----	-----	-----	-----

Find :

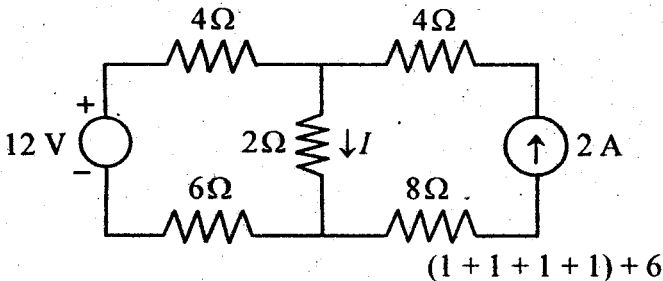- (i) Complete incidence matrix
 - (ii) Without drawing the connected graph, the branches in series and also in parallel
 - (iii) Whether branches (1, 4, 5) form a tree or not.
- (b) For the network as shown in the figure find the current ' I ' through the 2Ω resistance using Thevenin's theorem



3. (a) Draw the pole-zero diagram of the following system function

$$H(s) = \frac{5s(s^2 + 5s + 6)}{(s + 1)(s^2 + 3s + 9)}$$

- (b) Following test data were obtained for an unknown two-port network experimentally. Obtain the Y -parameters.

Status of circuit	V_1	V_2	I_1	I_2
Output shorted	25 V	0	5 mA	0.2 mA
Input shorted	0	30 V	6 mA	3 mA

5 + 5

4. (a) A T section low pass filter has a series inductance 80 mH and shunt capacitance 0.022 μ F. Determine the cut-off frequency and nominal design impedance R_0 . Also design an equivalent Π section.

- (b) Design a high pass active filter of cut-off frequency 1 kHz with a pass-band gain of 2.

5 + 5

5. (a) The driving point impedance of an L - C network is given by

$$Z(s) = \frac{5(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

obtain Foster first form of network inserting the values of all the elements.

- (b) The driving point impedance of a R - C network is given as

$$Z(s) = \frac{(s + 1)(s + 3)}{s(s + 2)}$$


obtain Cauer any of the two forms of network and insert the values of the elements. 5 + 5

6. (a) Find the convolution integral where $f_1(t) = e^{-at}$ and $f_2(t) = t$.
- (b) Find the final value of the function whose Laplace Transform is,

$$I(s) = \frac{s+6}{s(s+3)}$$

check the result by solving it for $i(t)$.

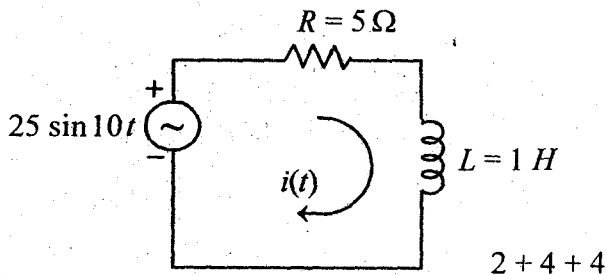- (c) A sinusoidal voltage $25 \sin 10t$ is applied at $t = 0$ to a circuit as shown in the figure. By the method of Laplace transform find the current $i(t)$. Initial conditions are taken to be zero.



[Internal Assessment : 10 Marks]