

**M.Sc. 1st Semester Examination, 2012****ELECTRONICS***( Electronic Circuit Lab )**( Practical )*

PAPER—ELC-106

*Full Marks : 50**Time : 3 hours*

Answer any **one** question, selecting it by a lucky draw  
*The figures in the right-hand margin indicate marks*

1. Design a regulated power supply using 78xx group of IC regulator and study its performance.

Output Voltage = ... V,

Output Current = ... mA.

- |   |       |
|---|-------|
| (a) Working formula.  | 4     |
| (b) Drawing of circuit diagram with labelling.                                      | 3     |
| (c) Circuit implementation on bread board.  | 3     |
| (d) Recording of data for getting the characteristics of load and line regulations. | 5 + 5 |
| (e) Drawing of graphs.  | 4 + 4 |
| (f) Calculation of percentage regulation and stability factor.                      | 2 + 2 |
| (g) Discussion of the results obtained.   | 3     |

*( Turn Over )*

2. Design a regulated power supply of variable output using LM 317

Output Voltage = 5V to 7.5 V

Output Current = 100 mA.

- |  |       |
|--|-------|
| (a) Working formula.   | 4     |
| (b) Circuit diagram with labelling.                            | 3     |
| (c) Circuit implementation on bread board.                     | 3     |
| (d) Recording of data for load and line regulations.           | 5 + 5 |
| (e) Drawing of graphs.   | 4 + 4 |
| (f) Calculation of percentage regulation and stability factor. | 2 + 2 |
| (g) Discuss of the results obtained.                           | 3     |

3. Design a regulated power supply using a power transistor as a pass element and an OPAMP as comparator.

Output Voltage = ... V, Output Current = ... mA.

- |   |       |
|---|-------|
| (a) Working formula.  | 4     |
| (b) Circuit diagram with labelling.                                 | 3     |
| (c) Design considerations and components to be used.                | 4     |
| (d) Circuit implementation on bread board.                          | 4     |
| (e) Recording of data for load and line regulation characteristics. | 4 + 4 |
| (f) Drawing of graphs.  | 3 + 3 |
| (g) Calculation of percentage regulation and stability factor.      | 2 + 2 |
| (h) Discussion of the results obtained.                             | 2     |

4. Design a regulated power supply using a power transistor as a pass element and another transistor as a comparator.

Output Voltage = ... V, Output Current = ... mA.

- |   |       |
|---|-------|
| (a) Working formula.  | 4     |
| (b) Circuit diagram with labelling.                                 | 3     |
| (c) Design considerations and components to be used.                | 3     |
| (d) Circuit implementation on bread board.                          | 3     |
| (e) Recording of data for load and line regulation characteristics. | 4 + 4 |
| (f) Drawing of graphs.  | 4 + 4 |
| (g) Calculation of percentage regulation and stability factor.      | 2 + 2 |
| (h) Discussion of the results obtained.                             | 2     |

5. Study the performance of a logarithmic amplifier using OPAMP.

- |  |       |
|--|-------|
| (a) Working formula.   | 4     |
| (b) Circuit diagram with labelling.  | 3     |
| (c) Implementation of the circuit on bread board.                              | 3     |
| (d) Recording of data by varying the input voltage at small steps.             | 10    |
| (e) Drawing of graphs.   | 4 + 4 |
| (f) Discuss the nature of graphs obtained and also the results.                | 3     |
| (g) Comment on possible application of the circuit using the results obtained. | 4     |

6. Study the performance of an antilogarithmic amplifier using OPAMP.
- |   |       |
|---|-------|
| (a) Working formula.  | 4     |
| (b) Drawing of circuit diagram with labelling.                      | 3     |
| (c) Circuit implementation on bread board.                          | 3     |
| (d) Recording of data by varying the input voltage at small steps.  | 10    |
| (e) Drawing the graphs.   | 4 + 4 |
| (f) Discussion about the nature of curves and the results obtained. | 3     |
| (g) Comment on possible application of the circuit.                 | 4     |
7. Design an active low pass Butterworth filter with a roll off rate 20 dB/decade having cut off frequency 2 kHz and pass-band gain of 2. Study its performance.
- |   |   |
|---|---|
| (a) Working formula.  | 4   |
| (b) Circuit diagram with labelling.   | 3   |
| (c) Design considerations and components to be used.  | 4   |
| (d) Implementation of the circuit on bread board.   | 3   |
| (e) Recording of data for frequency response characteristics.                               | 8   |
| (f) Drawing of graphs.  | 4   |
| (g) Finding and comparison of cut off frequency and Roll off rate with the supplied values. |   |
|   | $(2 + 1\frac{1}{2}) + (2 + 1\frac{1}{2})$ |
| (h) Discussion of the results obtained.   | 2   |

8. Design an active high pass Butterworth filter at a cut off frequency of 3 kHz and pass band gain of 2 using only one R-C section and study its performance.
- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design considerations and components to be used. 4
- (d) Implementation of the circuit. 3
- (e) Recording of data for frequency response characteristics. 8
- (f) Drawing of graph. 4
- (g) Finding and comparison of the cut-off frequency and Roll off rate with the given values.  $(2 + 1\frac{1}{2}) + (2 + 1\frac{1}{2})$
- (h) Discussion of the results obtained. 2
9. Design a second order active low pass Butterworth filter and study its performance.
- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design considerations for cut off frequency = ... kHz. 5
- (d) Implementation of the circuit on bread board. 3
- (e) Recording of data for frequency response characteristics. 8
- (f) Drawing of graph. 4
- (g) Finding and comparison of the Cut off frequency and Roll off rate with the known values.  $(2 + 1) + (2 + 1)$
- (h) Discussion of the results obtained. 2

10. Design a second order active high pass Butterworth filter and study its performance.

- |  |                   |
|--|-------------------|
| (a) Working formula.   | 4                 |
| (b) Circuit diagram with labelling.  | 3                 |
| (c) Design considerations for cut off frequency = ... kHz.                                       | 5                 |
| (d) Implementation of the circuit on bread board.  | 3                 |
| (e) Recording of data for frequency response characteristics.                                    | 8                 |
| (f) Drawing of graph.  | 4                 |
| (g) Finding and comparison of the Cut off frequency and the Roll off rate with the known values. | (2 + 1) + (2 + 1) |
| (h) Discussion of the results obtained.  | 2                 |

11. Design a R-C coupled amplifier using transistors and study its performance.

- |   |    |
|---|----|
| (a) Working formula.  | 4  |
| (b) Circuit diagram with labelling.                           | 3  |
| (c) Design considerations for gain = ...                      | 5  |
| (d) Implementation of the circuit on bread board.             | 3  |
| (e) Recording of data for frequency response characteristics. | 10 |
| (f) Drawing of graph.   | 4  |
| (g) Calculation of band width.                                | 3  |
| (h) Discussion of the results obtained.                       | 3  |

Distribution of Marks

Laboratory Note Book	:	5
Viva Voce	:	10
Experiment	:	35
		<hr/>
		50