

**2017**

**ELECTRONICS**

*( Basic Circuit Theory and Network Analysis )*

**[ Honours ]**

**( CBCS )**

**[ First Semester ]**

**PAPER – C1T**

*Full Marks : 40*


*Time : 2 hours*

*The figures in the right hand margin indicate marks  
Candidates are required to give their answers in their  
own words as far as practicable*

*Illustrate the answers wherever necessary*


1. Answer any *five* questions from the following : 2 × 5
- (a) A sinusoidal voltage is represented by  
 $v = 141.4 \sin(314.18 t - 90^\circ)$ . Find the r.m.s.  
value and frequency of the voltage.

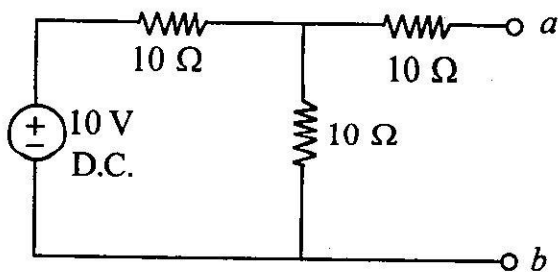- (b) Find the thevenin's voltage and resistance of the following circuit as seen resistance of the following circuit as seen at  $a - b$ .




- (c) Three resistances  $4 \Omega$ ,  $6 \Omega$  and  $8 \Omega$  are connected in parallel. In which resistor power dissipation will be maximum and why?
- (d) What do you mean by active and passive network elements? Give suitable examples.
- (e) If the impedance of an inductive coil is  $Z = (5 + j 10) \text{ ohm}$ , find conductance of the coil.
- (f) Explain how  $Q$  acts as an amplification factor in resonant circuit?

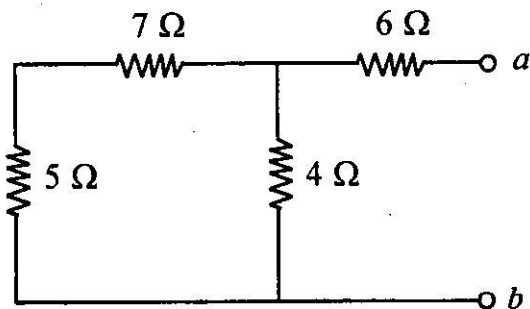- (g) Find the equivalent resistance across the terminals  $a$  &  $b$ .



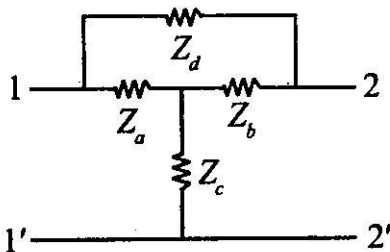
- (h) Convert the following circuit to a T Network.




2. Answer any *four* questions from the following : 5 × 4

- (a) Find the circuit in each branch of the network using Kirchhoff's laws.


( 4 )

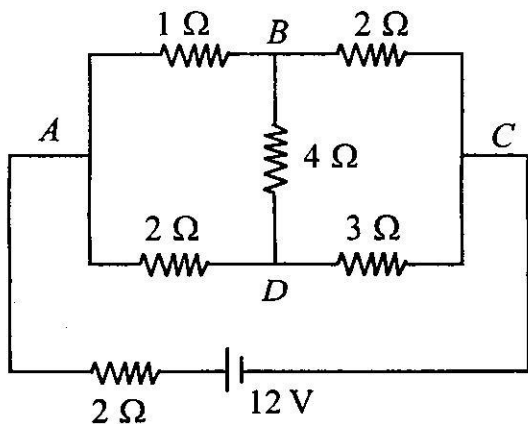

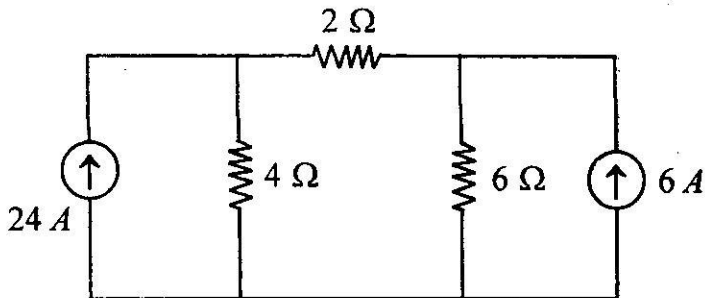- (b) State and prove the maximum power transfer theorem
- (c) Applying superposition theorem, compute the current through the  $2\ \Omega$  resistor in the following circuit.



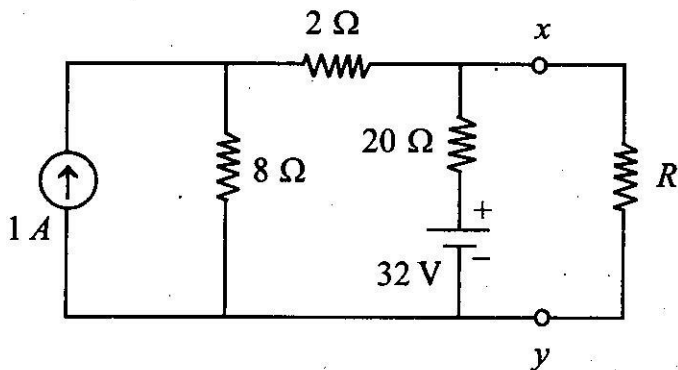- (d) Prove that the current in purely capacitive circuit leads the applied voltage by an angle  $90^\circ$  and draw their waveforms. Also calculate the average power of capacitive circuit.
- (e) Find the Thevenin's equivalent circuit of the following figure between the terminals  $x-y$ .



- (f) For a two port reciprocal Network prove that  $AD - BC = 1$


3. Answer any *one* question :

10 × 1

- (a) Define  $Q$  and give its expression for an inductor and a capacitor. Explain how the  $Q$  of a coil varies with frequency.

The following circuit is driven by a current source  $i = 4\sqrt{2} \sin 2t$  A and is in the steady state. Find the impedance faced by the current source and the power dissipated.

$$2 + (2 + 2) + 1 + 3$$

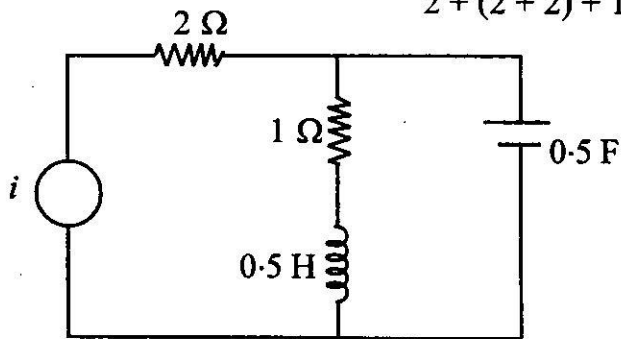

- (b) (i) Explain Delta  $\Delta$  – star (Y) conversion and star (Y) – Delta ( $\Delta$ ) conversion, for a purely resistive circuit.

$$2\frac{1}{2} + 2\frac{1}{2}$$

- (ii) Reduce the network given in the next

page of obtain the equivalent resistance  
as seen between nodes *cd*.

5

