

**M.Sc. 3rd Semester Examination, 2011**

**PHYSICS**

*Full Marks : 40*

*Time : 2 hours*

*The figures in the right hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

Special Paper : ( *Analog Elec.* )

PAPER — PHS - 304A

[ *Marks : 20* ]

Answer **Q. No. 1** and any **one** from the rest

1. Answer any *five* bits : 2 x 5

(a) Explain how a phase locked loop can be used as FM demodulator.

( *Turn Over* )

- (b) Draw the circuit diagram of a simple instrumentation amplifier using one op-amp and mention its demerits.
  - (c) Explain the advantages of bridge amplifiers over single stage amplifiers.
  - (d) Why regulated power supply is necessary for electronic instruments like public address system ?
  - (e) Explain how an analog multiplier can be used as an analog phase detector.
  - (f) Explain how a band reject filter can be designed using a given low pass filter and a high pass filter. What is the necessary condition ?
  - (g) Draw the circuit diagram of a voltage controlled oscillator.
2. (a) Draw and explain the circuit diagram of a logarithmic amplifier using matched pair of transistor and derive the expression for the output voltage in terms of input voltage.

- (b) Draw the circuit diagram of a 2nd order low pass Butterworth filter and derive the expression for the transfer function as a function of frequency. 1 + 4
3. (a) Draw the circuit diagram of a triangular wave generator using op-amps and explain its circuit operation with proper diagram of output voltages. Derive an expression for the frequency of oscillation. 5
- (b) Explain the operation of a switching regulator and state the merits of it over series regulators. 5

Special Paper : ( *Digital Elec.* )


PAPER – PHS - 304B

[ *Marks : 20* ]

Answer Q. No. 1 and any one from the rest

1. Answer any *five* bits : 2 x 5
- (a) Design a C-MOS transmission gate.
- (b) Define 'figure of merit, and compare it for TTL and ECL gates.

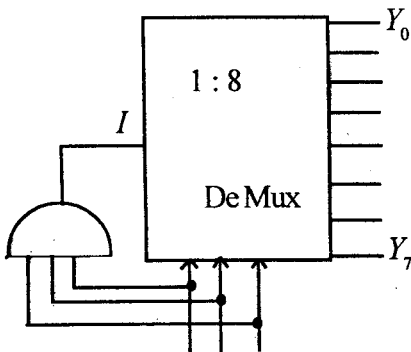(c) What will be the outputs for different selectors ?



(d) Solve  $Y = A\bar{B} + \bar{A}B$  by FPLA circuit.

(e) Differentiate SRAM from DRAM.

(f) State the principle of optical memory.

2. (a) Describe the operation of 4 phase dynamic shift register. 4

(b) Give the circuit diagram of DRAM unit cell. How it is advantageous over SRAM unit cell ? 2 + 1

(c) What do you mean by MBM ? Mention two distinct differences of MBM from CCD. 2 + 1

3. (a) Design a two input TTL NOR gate or three input ECL OR/NOR gate. 3
- (b) Explain the operation of three input NMOS NAND gate with proper circuit diagram. 3
- (c) State different uses of multiplexer circuit. 2
- (d) Show how TTL gate works as current source and current sink. 2

Special Paper : ( *Solid State* )

PAPER – PHS - 304

[ *Full Marks : 40* ]

Answer Q. No. 1 and any **three** from the rest

1. Answer any *five* bits : 2 x 5
- (a) What is screw dislocation ?
- (b) Find the bandwidth in a bcc crystal along [111] direction according to Tight Binding Approximation.

- (c) Explain how dislocation increases plasticity in a solid.
  - (d) Find the shortest burger vector corresponding to stable dislocation in a FCC crystal.
  - (e) What are the essential conditions of a material to be ferroelectric ?
  - (f) Show the variation of mobility for a non-degenerate semiconductor in the low temperature region.
  - (g) Prove that thermal entropy change in a perfect crystal is zero.
  - (h) What is Polariton ?
2. (a) Derive the energy dispersion relation for an electron in a solid according to nearly free electron approximation. 8
- (b) Show that energy discontinuity occurs at zone boundary. 2
3. (a) Derive the LST relation assuming phonon-photon interaction in an ionic crystal. 8
- (b) What is Mott's Metal-Insulator transition ? 2

4. (a) Discuss in details the Landau theory of phase transition for  $\text{BaTiO}_3$  crystal. 6
- (b) What is meant by Polarization Catastrophe? 2
- (c) What is meant by dielectric relaxation? 2
5. Derive the Landau levels in case of metal placed in a magnetic field at low temperature. 10
6. Derive Boltzmann transport equation and hence find an expression for conductivity in a non-degenerate semiconductor. 10
-