

M.Sc. 3rd Semester Examination, 2012

PHYSICS

PAPER — PHS-304

Full Marks : 40

Time : 2 hours

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

PAPER — PHS-304

(Special Paper : Solid State Physics)

[Marks : 40]

Time : 2 hours

Answer Q. No. 1 and any three from the rest

1. Answer any five bits : 2 × 5

(a) Explain what is meant by Plasmon.

(Turn Over)

- (b) Find the bandwidth in simple cubic crystal along [110] direction according to tight binding approximation.
- (c) Explain what is meant by F-center.
- (d) The average energy required to create a Frenkel defect in an ionic crystal, $A^{2+} B^{2-}$, is 1.4 eV. Calculate the ratio of Frenkel defects at 300 K and 600 K in 1 gm of crystal.
- (e) Calculate the Burger vector in Aluminium crystal. Lattice constant is $a = 4.05 \text{ \AA}$.
- (f) Explain what is meant by complex dielectric constant.
- (g) Plot screened and unscreened Coulomb potential of a unit positive charge as seen by an electron in a solid.
2. (a) Derive the energy of electron in a solid according to T.B.A. 8
- (b) Explain what is meant by reduced zone scheme. 2

3. (a) Derive the expression of Thomas Fermi dielectric function assuming screening behaviour of electron gas in a metal. 8
- (b) What is Thomas Fermi Screening length? 2
4. (a) Describe in detail the dipole theory of Ferroelectricity. 5
- (b) Derive an expression of A.C. polarizability assuming frequency dependence of dipolar polarizability in a dielectric. 5
5. (a) Derive an expression for conductivity in an ionic crystal. 5
- (b) Find an expression for dislocation energy of a screw dislocation. 5
6. (a) Derive the dispersion relation corresponding to Frenkel exciton. 5
- (b) Describe in detail de Hass-van Alphen effect. 4
- (c) What is meant by ultraquantum region. 1

(**Special Paper : Applied Electronics**)

PAPER – PHS-304 A

[*Marks : 20*]

Time : 2 hours

Answer Q. No. 1 and any one from the rest

1. Answer any *five* bits : 2 × 5

- (a) Explain with circuit diagram, how a bridge amplifier can be used as a transducer.
- (b) Discuss about the advantages of active filters over passive ones.
- (c) Draw the circuit diagram of an antilog amplifier using matched pair of transistors and OP-AMP.
- (d) Design a 2nd order high-pass Butterworth filter with cut-off frequency of 10 kHz.
- (e) Explain the advantages of switching regulators over series regulators.

- (f) Draw the circuit diagram of a four quadrant analog multiplier using transistor and OP-AMP. State one of its uses.
- (g) Why a logarithmic amplifier cannot be used for very low and very high input voltages ?
2. (a) What do you mean by an instrumentation amplifier ? Draw the circuit diagram of an instrumentation amplifier using 3-OP-AMPs and derive the expression for the output voltage. 1 + 4
- (b) Draw the block diagram of a Phase Locked Loop and describe its operation. 1 + 2
- (c) Explain the use of an Ex-OR gate as a digital phase detector. 2
3. (a) Explain the circuit operation of an inverting Schmitt trigger and find out an expression for the hysteresis voltage. 5
- (b) How the circuit of a Schmitt trigger can be changed to design a voltage controlled oscillator and derive the expression for the output frequency. 5

PAPER – PHS-304 B

[Marks : 20]


Time : 2 hours

Answer Q. No. 1 and any one from the rest

1. Answer any five bits : 2 × 5

(a) Why ECL is faster than TTL ?

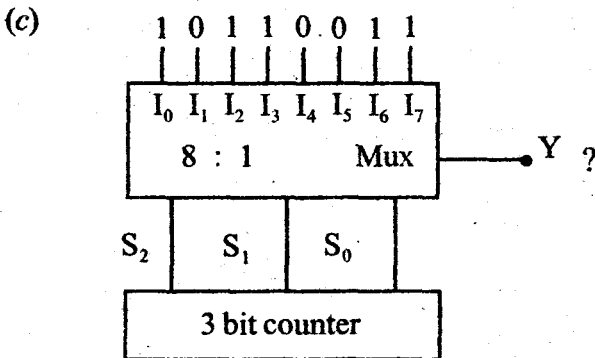(b) Draw the circuit of 2 input C-MOS NAND gate.



Draw the output waveform.

(d) Draw the unit cell of SRAM.

(e) State the working principle of optical memory in compact disk.

(f) Establish the relation of flip-flop, register and memory cell.

2. (a) State briefly the working principle of 3-phase CCD unit. 3

(b) What do you mean by "field programmable logic array"? Give example. 3

(c) Show the circuit diagram of "two-phase ratioless dynamic shift" register. 3

(d) (32 K × 16) memory IC has data line and address line. Complete the above sentence. 1


3. (a) Solve the following equation by 8 : 1 Multiplexer IC :

$$Y = \sum m(2, 5, 7, 9, 12, 13). \quad 3$$

(b) Design TTL tri-state inverter logic gate and show the three different states. 3

- (c) What do you mean by propagation delay?
Considering propagation delay show the output
of the following circuit :

3

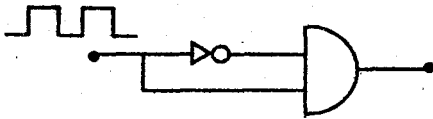

- (d) What is VLSI?

1
