

M.Sc. 1st Semester Examination, 2012

PHYSICS

PAPER — PHS- 104(A + B)

Full Marks : 40

Time : 2 hours

*The figures in the right hand margin indicate marks
Candidates are required to give their answers in their
own words as far as practicable*

Illustrate the answers wherever necessary

**Write the answers to questions of each Group
in separate books**

GROUP — A

[Marks : 20]


Time : 1 hour

Attempt **Q.No.1** and any **one** from the rest


1. Attempt any *five* bits : 2 × 5

(a) What is fading in radio wave communication ?

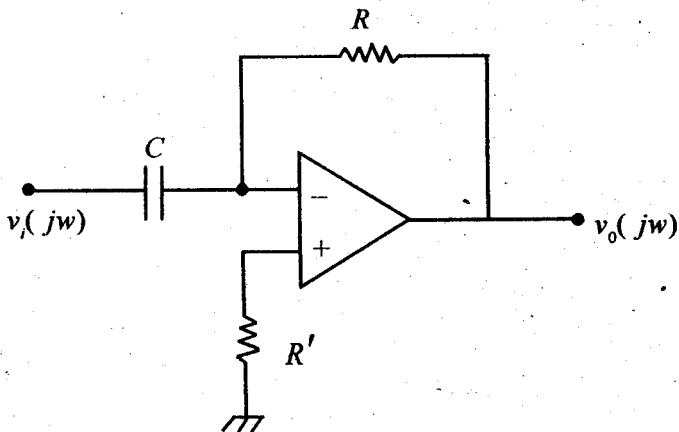- (b) What do you mean by slew rate of an Op-Amp? What should be its ideal and practical value?
- (c) Compute the length of a $\lambda/2$ antenna required to transmit an FM signal at a frequency of 100 MHz.
- (d) Explain the terms Ground wave and sky wave in case of radio wave propagation.
- (e) Write down the expression for the refractive index of ionosphere, with explanations of the different terms used.
- (f) Find $v_o(j\omega)$ in terms of $v_i(j\omega)$ for the following Op-Amp circuit



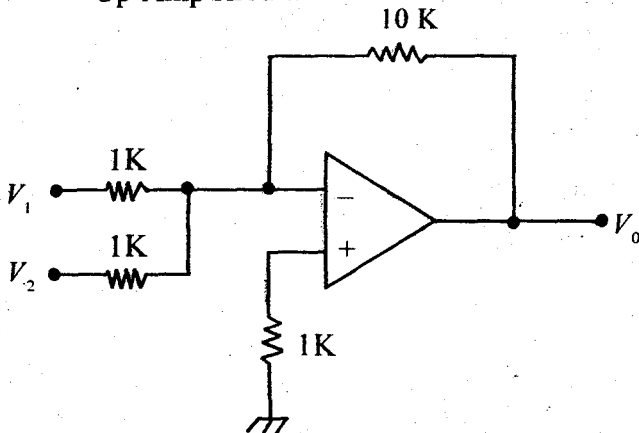- (g) Find the value of the O/P voltage of the following Op-Amp circuit.



$$V_1 = 0.2V, V_2 = 0.5V$$

2. (a) What do you mean by frequency modulation? Write down the expression for the FM wave modulated by a sinusoidal signal and find out its spectral components. Hence find out the theoretical bandwidth of FM. 1 + 1 + 3 + 1
- (b) Draw the circuit diagram of any type of FM modulator and derive the necessary theory of operation. 1 + 3

3. (a) Derive RADAR range equation in free space. Hence explain how RADAR range can be increased? 5 + 1
- (b) Explain the working principle of Doppler RADAR. 3
- (c) What is the difference between CW radar and pulsed radar? 1

GROUP – B

[Marks : 20]

Time : 1 hour

Answer Q.No.1 and any one from the rest

1. Answer any five questions : 2 × 5
- (a) Represent the following function of A, B, C by Karnaugh map :
- $$F(A, B, C) = AB + C$$
- (b) Draw the Karnaugh map of
- $$F(A, B, C, D) = \sum m(2, 3, 6, 7, 10, 11, 14, 15)$$
- (c) What is a decade counter? How can it be designed?

- (d) A clock pulse of 8 kHz is applied in the clock input of a 3-bit asynchronous counter. Find the frequency of the outputs of its different flip-flops.
- (e) What is a seven segment display ? What are the different kinds of seven-segment display are there ?
- (f) Write the advantage of serial-in parallel-out shift register over serial-in serial-out one.
- (g) Draw the block diagram of 555 timer.

2. (a) What is an astable multivibrator ? Discuss the principle of operation of the astable multivibrator using transistor. Discuss, why it is called a self triggering circuit.
- (b) Obtain the expression of frequency of oscillation of the multivibrator. $1 + 4 + 2 + 3$

3. (a) Draw the circuit diagram of a JK-flip-flop using NAND gates only and explain its operation. $2 \frac{1}{2} + 2 \frac{1}{2}$
- (b) What is race-around condition ? How this condition is eliminated ? $2 + 3$
-