

**M.Sc. 2nd Semester Examination, 2010**

**PHYSICS**

**PAPER — PH-1204 (A + B)**

*Full Marks : 40*

*Time : 2 hours*

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

**GROUP—A**

*[Marks : 20]*


1. Answer any *five* questions from the following : 2 × 5

(a) Why a photo diode is never used in forward bias ?

(b) Define image impedance pair of a network.


(Turn Over)

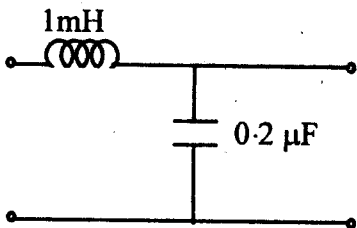- (c) Find the cut-off frequency of the following filter and write the nature of the filter.



- (d) What is a transmission line and draw its equivalent circuit?

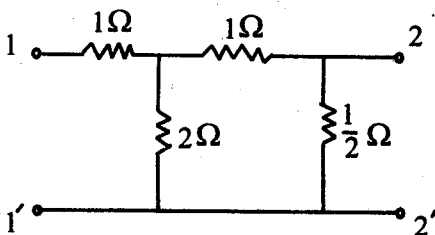- (e) Find the  $Z$  parameter of the following circuit.



- (f) When can you call a ' $T$ -network' symmetric? Write the expression of characteristic impedance of the symmetric  $T$ -network.


(g) If  $Z$  and  $Y$  are the series impedance and shunt admittance per unit length of a transmission line, then write the expressions of the characteristic impedance and propagation constant in terms of  $Z$  and  $Y$ .

(h) By what type of materials does a photo-conductor developed? How does its conductivity depend on the incident light intensity on it?

2. Answer any *one* questions :

10 × 1

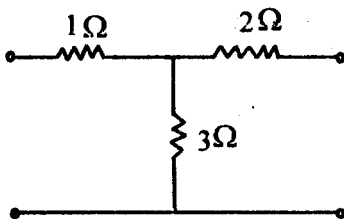(a) (i) Convert the following  $T$ -network into its equivalent  $\pi$  form and derive the necessary formulae.



(ii) Design a constant- $k$  high pass filter having cut-off frequency of 10 kHz and derive the expression for cut-off frequency. 5 + 5

- (b) (i) Obtain the expression of voltage and current equations of a transmission line.
- (ii) Using the above equation find also the expression of reflection co-efficient of the line.
- (iii) Discuss the principle of cable fault location of a telephone line with supporting equation. 5 + 2 + 3

GROUP—B

[Marks : 20]

Answer Q.No.1 and any *one* from the rest

1. Attempt any *five*: 2 × 5
- (a) Give the basic block diagram of an ALU. Mention the operations it executes.
- (b) Give the idea of addition of two signed binary numbers.
- (c) What are the different status flag? How many bits are allocated for each status flag?

- (d) What is the basic differences between SRAM and DRAM?
- (e) What is the value of *B* register after the execution of the following programme ?

```
XRA A
MVI D 10
ADD D
MOV BA
HLT
```

- (f) Draw the architecture of a basic bipolar memory cell using multiemitter bipolar transistors.
- (g) What is pulse code modulation? Write one advantage of this modulation over other pulse modulation schemes.
- (h) What is the method of recording information in a magnetic memory?
2. (a) Give the neat block diagram of an ADC system. 3
- (b) Explain the idea of getting T.D.M in PAM system. 3
- (c) With supporting diagram discuss the function of a dynamic MOS RAM cell. 4

3. (a) What is accumulator? 2
- (b) What do you mean by machine language and mnemonics? 2
- (c) What are the function of the following pins in 8085  $\mu$ P?
- (i) TRAP
- (ii) SID 2
- (d) Three numbers are stored in memory location  $X$  onwards. Write a program for 8085  $\mu$ P to arrange the numbers in reverse direction i.e. the last number should be stored in first position and so on. 4
-