

M.Sc. 2nd Semester Examination 2014**PHYSICS**

PAPER – PHS-204(Gr.-A + Gr.-B)


*Full Marks : 40**Time : 2 hours*

*The figures in the right hand margin indicate marks
Candidates are required to give their answers in their
own words as far as practicable*

Illustrate the answers wherever necessary


GROUP—A**[Marks : 20]****Answer Q.No.1 and any one from the rest****1. Attempt any five of the following : 2×5**

(a) Convert the following T network into its equivalent π -network

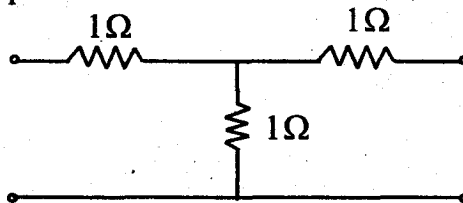**(Turn Over)**

(2)

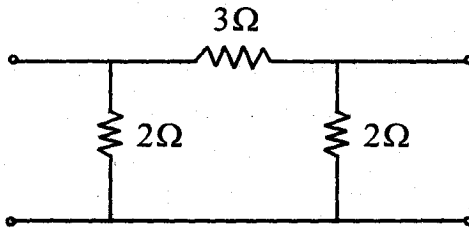- (b) Define the terms reflection coefficient and voltage standing wave ratio in case of a transmission line.
- (c) Find the characteristic impedance of the following π -network.



- (d) Explain the origin of distortion in a transmission line.
- (e) Draw the equivalent circuit of a transmission line using primary line constants.
- (f) Design a constant k low pass filter having the following specifications –

Nominal resistance = 500Ω

Cut-off frequency = $1000/\pi$ Hz.

(3)

(g) Explain in short the basic principle of operation of a phototransistor.

(h) Why a photodiode is never used in forward bias mode ?

2. (a) Sketch the frequency response characteristics of an ideal band-pass filter. 1

(b) Draw the circuit diagram of a constant- k -band-pass filter and derive the expressions for its cut-off frequencies. Derive the expressions for attenuation constant and phase constant in the pass band and attenuation band. Also represent graphically their variations as a function of frequency in the pass band and attenuation band.

1 + 3 + 4 + 1

3. (a) State and explain the two corollaries of Foster's reactance theorem. 4

(b) Draw the cross-sectional diagram of a silicon controlled rectifier and its two transistor equivalent circuit. Is it possible to fabricate similar type of device using germanium ?

1 + 1 + 2

(4)

- (c) Draw the $I-V$ characteristic of a Triac, with proper labelling of the different voltages and currents.

2

GROUP-B

[Marks : 20]

Answer Q.No.1 and any one from the rest

1. Answer any five bits : 2 × 5

(a) What do you mean TDM-PAM ?

(b) An analog signal is represented by the equation

$$x(t) = 3 \cos(50 \pi t) + 10 \sin(300 \pi t) - \cos(100 \pi t).$$

Calculate the Nyquist rate for this signal.

(c) What is EEPROM ?

(d) Draw the basic memory cell for ROMs using diodes.

(e) Multiply $(110101)_2$ by $(1101)_2$.

(5)

- (f) What is floating-point binary representation ?
Explain with an example.
- (g) Write the meaning of the following instructions for a 8085 μp – LHLD addr. ; STAX B ; DAD ; XCHG.
- (h) Write a programme which subtracts two numbers $5A_H$ and FF_H through immediate addressing.
2. (a) Design a 1-bit comparator circuit having three outputs ($A > B$), ($A = B$) and ($A < B$) using only 2-input NAND-gates. 3
- (b) Write the function of stack-pointer, temporary-register and Instruction-register in connection with a 8085 μp . 3
- (c) What are the important properties that characterize the memory used in digital computer ? What are the differences between SRAM and DRAM ? 4
3. (a) What is a multiplexer ? Design a 4 : 1 multiplexer using basic-gates. 1 + 3

(6)

- (b) What do you mean by Pulse-width-modulation (PWM) and pulse-position-modulation (PPM) method ? 3
- (c) What do you mean by quantization error in PCM method ? How do you improve the error ? 3
-