

M.Sc. 2nd Semester Examination, 2025

PHYSICS

(Digital Electronics)

PAPER – PHS-207

Full Marks : 25

Time : 1 hour

Answer all questions

The figures in the right hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

GROUP – A

1. Answer any two questions : 2 × 2

(a) What is the data writing process of a compact disk memory ?

(Turn Over)

- (b) Differentiate machine language, opcode and mnemonics.
- (c) Draw a circuit which can add or subtract two 2-bit binary numbers.
- (d) In a 6-bit DAC the full swing is 0V to 21V. What will be the output voltage for the input 100001? What is the resolution of the DAC?

GROUP – B

2. Answer any two questions : 4 × 2

(a) (i) Design 8:1 multiplexer to get the output waveform 10010010.

(ii) What is the difference between SRAM and DRAM? 2 + 2

(b) (i) Give the schematic of A.L.U. and explain the function of it.

(ii) Consider a 2-bit carry look ahead adder. Draw the circuit to generate the carry C_2 . 2 + 2

(c) (i) Give the result of the following execution; $(2B)_H$ EXOR $(C1)_H$ and $(2B)_H$ NAND $(C1)_H$.

(ii) Give the digital circuit of 2-bit multiplier. 2 + 2

(d) (i) What are the different FLAG registers in 8085 microprocessor ?

(ii) Give the role of different registers in 8085 microprocessor ? 2 + 2

GROUP - C

3. Answer any *one* question : 8 × 1

(a) (i) Draw the circuit to expand 16×4 memory IC to 32×8 memory cell.

(4)

(ii) Give the circuit diagram of a BCD Adder. 4 + 4

(b) (i) Schematically construct a 4-bit ADC and explain the function briefly.

(ii) Solve the digital equation $Y = \Sigma(2,3,7)$ using 8:1 Multiplexer. 4 + 4

[Internal Assessment – 5 Marks]
