

2025

M.Sc. 1st Semester Examination

ELECTRONICS

Paper : ELCC402X8

[Digital System Design]

(Practical)

Full Marks : 25

Time : Two Hours

Answer any *one* question by lucky draw.

1. Design and implementation of a half adder circuit.

- (a) Draw the logic diagram of the designed circuit using NAND or NOR gates.**
- (b) Construct the truth table for the half adder.**
- (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.**

2. Design and implementation of a full adder circuit.
 - (a) Draw the logic diagram of the designed circuit using NAND or NOR gates.
 - (b) Construct the truth table for the full adder.
 - (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.

3. Design and implementation of a 4 : 1 multiplexer circuit.
 - (a) Draw the logic diagram of the designed circuit.
 - (b) Construct the truth table for the 4 : 1 mux.
 - (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.

4. Design and implementation of a 1 : 4 demultiplexer circuit.
 - (a) Draw the logic diagram of the designed circuit.
 - (b) Construct the truth table for the 1 : 4 demux.
 - (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.

5. Design and implementation of a 2-bit magnitude comparator circuit.

- (a) Draw the logic diagram of the designed circuit.
- (b) Construct the truth table.
- (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.

6. Design and implementation of a 4-bit binary to Gray code converter.

- (a) Draw the logic diagram of the designed circuit.
- (b) Construct the truth table.
- (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.

7. Design and implementation of a JK flip-flop.

- (a) Draw the logic diagram of the designed circuit.
- (b) Construct the truth table.
- (c) Implement the circuit using appropriate ICs and verify the output for all possible input combinations.

8. Design and implementation of a 2-bit synchronous counter circuit.
 - (a) Design the logic diagram of the counter circuit.
 - (b) Construct the state table.
 - (c) Implement the circuit using appropriate ICs and verify the output states.

9. Design and implementation of a shift register.
 - (a) Draw the logic diagram of the designed circuit.
 - (b) Construct the state table.
 - (c) Implement the circuit using appropriate ICs and verify the output.

10. Design and implementation of a 4-bit R-2R ladder circuit.
 - (a) Draw the circuit diagram.
 - (b) Implement the circuit.
 - (c) Obtain the output voltage when 1000 input is applied to the circuit.

(5)

Evaluation Marks Distribution :

Laboratory Notebook	5
Viva-voce	5
Experiment	15
Total	25