

2013

DDE

**M.Sc. Part-I Examination**

**PHYSICS**

**PAPER—IV**

Full Marks : 75

Time : 3 Hours

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

**Write the answers Questions of each group in separate books.**

**Group—A**

[Marks : 40]

Attempt Q. No. 1, 2, 3 and any two from the rest.

1. Answer any five questions : 2×5


- (a) Explain why a constant current source is needed at the input stage of an operational amplifier.
- (b) Explain skip distance in radio wave communication.
- (c) Define a transitional line and draw its equivalent circuit.

(Turn Over)

- (d) What is Secant law in the case of radio wave propagation and what is its significance?
- (e) Explain the operation of a duplexer.
- (f) What are the advantages of photo transistor over photo diode?
- (g) Write down the expression for the refractive index of ionosphere with proper explanation of its different terms.
- (h) What should be the value of slow rate of an ideal OP-AMP? Why in a practical OP-AMP this value is not achieved?

2. Answer any *two* questions : 3×2

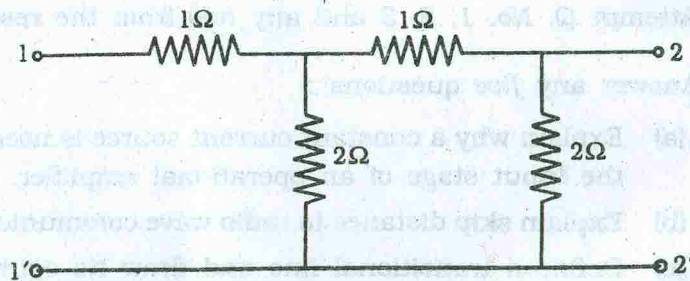- (a) A 2.5 kW carrier signal is amplitude modulated (DSB-TC) by a single frequency sinusoidal signal. If the modulation index is 70%, determine the total power of the modulated wave.
- (b) Find the Z-parameters of the following circuit :



- (c) Explain how a band stop filter can be realised by using a given high pass filter and low pass filter? What is the necessary condition?

3. Answer any *one* question : 4×1

- (a) Explain how the distance of a fixed target can be found by using two frequency CW Radar.
- (b) Discuss the phase cancellation method for generation of SSB signal.

4. (a) Draw the circuit diagram of a constant - k band pass filter and derive the expression for its cut-off frequencies. 1+3

- (b) Derive the expressions for  $\alpha$  and  $\beta$  in the pass band and attenuation band. Also graphically show their variations as a function of frequency in the pass band and in the attenuation band. 4+2

5. Derive telegrapher's equation and solve it to find the expression for voltage and current in a transmission line. Hence define the reflection co-efficient of a transmission line. 8+2

6. (a) Explain the realisation of a current mirror circuit using low  $\beta$  transistors and show that it will behave as a current mirror circuit with necessary derivation. 5

- (b) Explain how a given T-network can be converted into its equivalent  $\pi$  form with necessary derivation. 5


**Group—B**

[Marks : 35]


Attempt Q. No. 1, 2 and any two from the rest.

1. Answer any three bits : 3×2

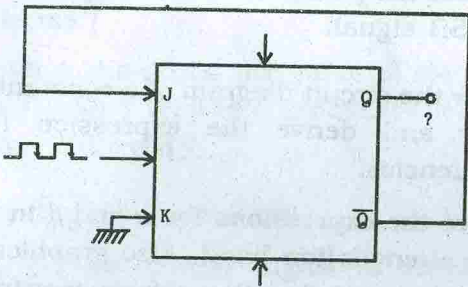
(a) What will be the output of the following circuit ?



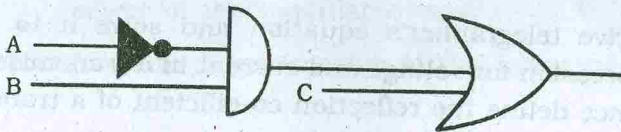(b) Design the following circuit with NAND gate only :



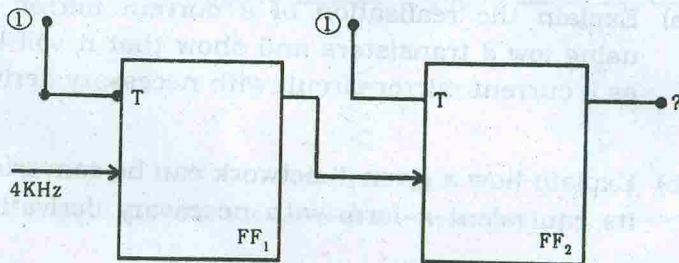(c) Draw the output wave form of the following circuit :



(d) Write down the differences between RAM &amp; ROM.

(e) What are the different flag registers in 8085  $\mu$ P ?2. Answer any three bits : 3×3

(a) Draw the circuit diagram of 3-bit synchronous counter and explain briefly.

(b) Solve the following equation with K' map :

$$Y = \prod M(0, 2, 5, 7, 10) \cdot d(12, 14, 15)$$

(c) Design a stable multivibrator circuit to produce square wave of  $\frac{2}{3}$  duty cycle.

(d) What is sampling theorem ? If a signal has frequency spectrum of (10 – 30) KHz and 5 KHz guard band is required then what will be the sampling frequency for that signal ?

(e) Explain the address and data bus operation in 8085  $\mu$ P.

3. (a) In a 4-bit input system the output is high when the LSB and MSB are in opposite phase. Draw the required Karnaugh map.

(b) Design a 3 bit bi-directional shift register and explain the working principle briefly.

(c) Design a circuit with primary gate to check whether two signal A ( $A_1A_0$ ) and B ( $B_1B_0$ ) are equal or not.3+4+3

4. Give the truth table in seven :
- Segment display for octal number system.
  - Describe the quantization and pulse code generation in PAM signal.
  - Give the circuit diagram for MOD-10 counter and explain briefly. 3+4+3
5. (a) What is sequential access memory? Explain with example.
- (b) What is a full adder circuit? Design the circuit of a full adder.
- (c) What do you mean by SID ; TRAP ; HOLD ; R/W ; pin in 8085  $\mu$ P?
- (d) What will be the output of B register after the execution of the following program? 3+3+2+2

```

MVI   A    0F
MVI   C    05
ADD   C
MOV   B    A
HLT

```