

**2016**

**M.Sc.**

**2nd Semester Examination**

**ELECTRONICS**

**PAPER—ELC-205**

**(PRACTICAL)**

*Full Marks : 50*

*Time : 3 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

**(Optoelectronics Lab)**

Answer any one question selecting it by a *lucky draw*.

1. Study the I (Current) – V (Voltage) characteristics of LED (Light emitting diode) of two colours and compare the results.

Allotment of Marks (A.M.)

- (a) Theory — 5
- (b) Circuit diagram — 2
- (c) Implementation of the circuit — 3
- (d) Data for I-V characteristics — 9+9
- (e) Graph — 5
- (f) Comparison of results and discussion — 2.

*(Turn Over)*

2. Find the numerical aperture of the given optical fibre. Calculate the acceptance angle of the same fibre.

Allotment of Marks

- (a) Working formula — 6
  - (b) Data for numerical aperture — 20
  - (c) Calculation of numerical aperture — 3
  - (d) Calculation of acceptance angle — 3
  - (e) Discussion of the results obtained — 3.
3. Study the Optical conversion of 4-bit digital signal to its analog form by R-2R ladder Network.

Allotment of Marks

- (a) Theory and working formula — 5
  - (b) Circuit diagram — 2
  - (c) Implementation of the circuit — 3
  - (d) Data for different digital inputs — 18
  - (e) Drawing of graph — 5
  - (f) Discussion of results obtained — 2.
4. Study the Current (I) - Voltage (V) characteristics of Light emitting diode of three colours and compare the results.

Allotment of Marks

- (a) Theory — 5
- (b) Circuit diagram — 2
- (c) Implementation of the circuit — 3
- (d) Data for I-V characteristics — 6+6+6

- (e) Graph — 5
  - (f) Comparison of results and discussion — 2.
5. Draw the characteristics of the given Voltage LDR for two light intensities. Calculate LDR resistances for both cases and compare accordingly.

Allotment of Marks

- (a) Theory and working formula — 5
  - (b) Circuit diagram — 2
  - (c) Implementation of the circuit — 3
  - (d) Data for characteristic curves — 14
  - (e) Graph — 5
  - (f) Calculation of LDR resistances — 2
  - (g) Comparison of resistances in the two cases and discussion about them — 4.
6. Study the frequency response of the given LDR.

Allotment of Marks

- (a) Theory — 5
- (b) Circuit diagram — 2
- (c) Implementation of the circuit — 3
- (d) Data for frequency response — 18
- (e) Graph — 5
- (f) Discussion — 2.

7. Given a slit with a hole of known diameter, determine the wavelength of light from diffraction of a laser beam.

Allotment of Marks

- (a) Working formula — 5  
 (b) Data for diffraction band on both sides of central band — 20  
 (c) Results and discussion — 10.
8. Given a slit with a hole of known diameter, determine the diameter of the hole from the diffraction of a laser beam of known wavelength.

Allotment of Marks

- (a) Working formula — 5  
 (b) Data for diffraction band on both sides of central band — 20  
 (c) Results and discussion — 10.

Marks Distribution

Experiment	:	35
LNB	:	05
Viva-Voce	:	10
<hr/>		
Total	:	50