

**2016****M.Sc.****1st Semester Examination****ELECTRONICS****PAPER—ELC-102***Full Marks : 50**Time : 2 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*


**(Network Analysis and Synthesis)**

Answer Q. No. 1 and any three questions from the rest.

1. (a) State Norton's theorem.
- (b) With a neat figure explain a two-port network. Give at least one example of a two-port network.

*(Turn Over)*

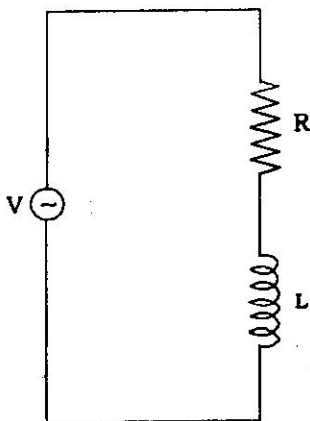- (c) Draw the phasor diagram of an R.L. circuit as given in the figure :



- (d) Design a filter with R and L to reject any noise above 20 Hz. Assume  $R = 100\Omega$ .
- (e) Define Laplace transform explaining the meaning of all symbols.


5×2

2. (a) The reduced incidence matrix of an oriented graph is :


$$[A] = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Draw the graph.

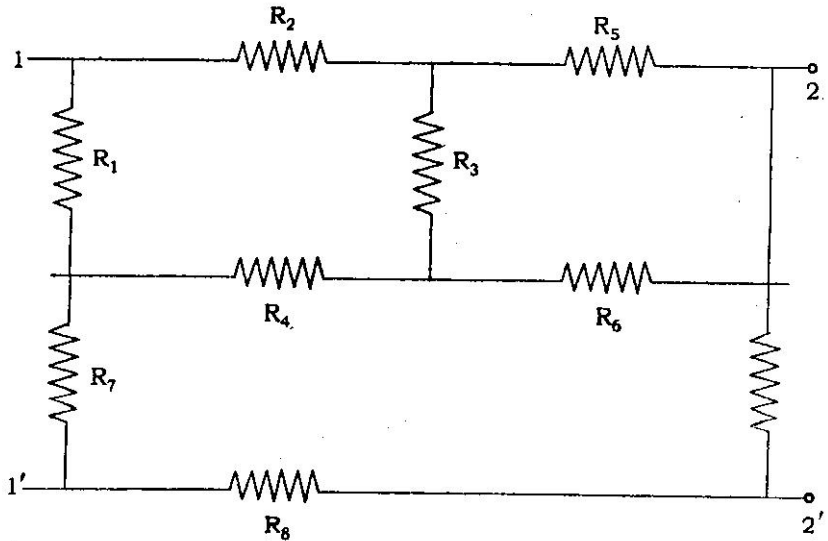(b) Reduce the following network to an equivalent T network :




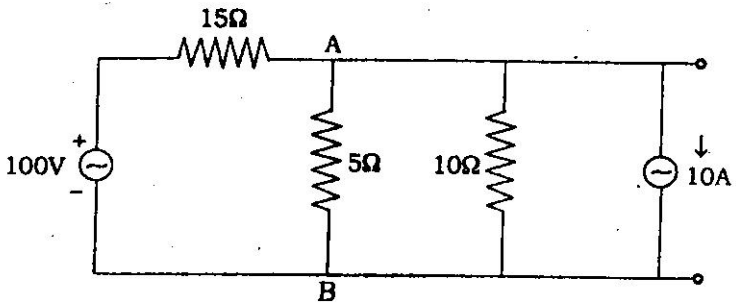(c) Use Thevenin's theorem to determine the current in the branch AB of the following circuit :




3+3+4

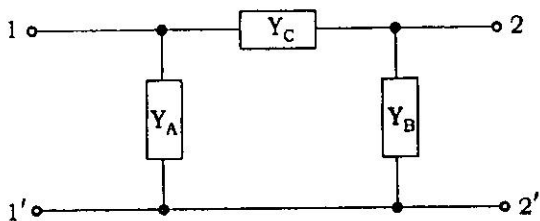3. (a) Determine the Y matrix of the following network :




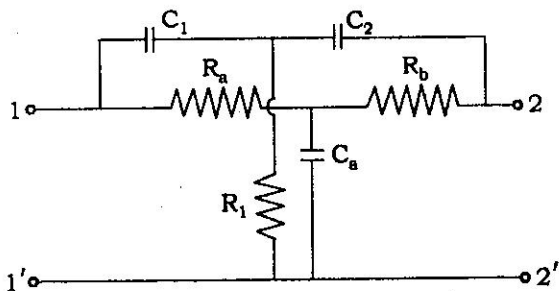- (b) For a reciprocal network prove that  $AD - BC = 1$ , where the symbols have their usual meanings.
- (c) Determine  $y_{11}$  of the following twin-T network :




3+4+3

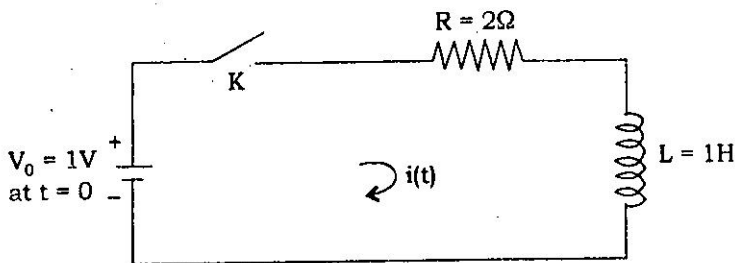4. (a) Consider the circuit shown below. The K switch is closed initially and it opens at  $t = 0$ . Determine current  $i(t)$  using Laplace transform :



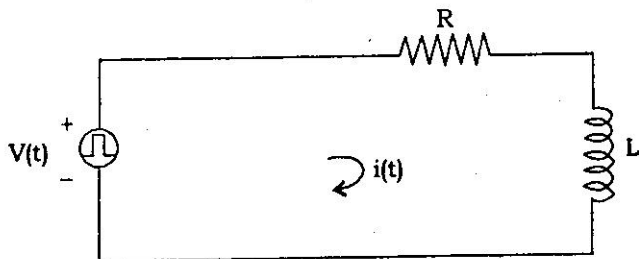- (b) A pulse of width  $a$  is applied to the following RL network at  $t = 0$ . Determine the current through the circuit.



- (c) Check whether the following function will be treated as a driving point impedance function or not :

$$Z(S) = \frac{4S^4 + S^2 - 3S + 1}{S^3 + 2S^2 + 2S + 40}$$


3+4+3

5. (a) Consider the function :


$$P(S) = (S + 1)(S + 2)(S + 3)(S + 4).$$

Indicate whether the function is stable using R-H theorem.

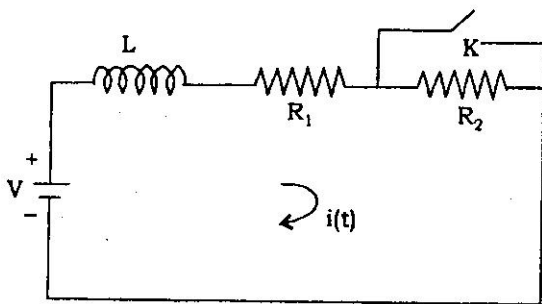(b) For the network circuit shown below, determine  $i(t)$  (i) when  $k$  is closed at  $t=0$ , (ii)  $k$  is opened at  $t=0$ :



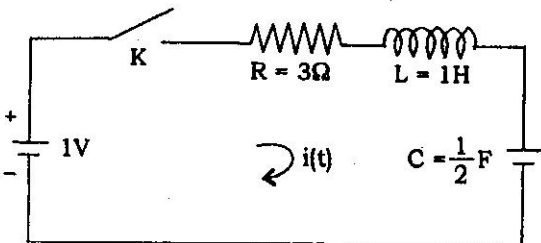(c) Determine  $i(t)$  for the following circuit.  $K$  is closed at  $t=0$  :



2+4+4

6. (a) The driving point impedance function of a Foster form is given by :

$$Z_D = j\omega H \left[ 1 + \frac{A_0}{\omega^2} + \frac{A_2}{\omega^2 - \omega_2^2} + \dots + \frac{A_k}{\omega^2 - \omega_k^2} + \dots \right]$$

Draw its equivalent network.

- (b) Determine the expression for the driving point impedance of a reactive network which has poles at  $\omega = 0$ , 4000 rad/sec and infinity. Zeros are to be located at  $\omega = 2000$  and 6000 rad/sec. The impedance is to be  $-j700$  ohm at 1000 rad/sec.
- (c) Derive the design equations for a low-pass constant-k filter.

3+3+4

**[Internal Assessment — 10 Marks]**

---