

2016

M.Sc.

4th Semester Examination

ELECTRONICS

PAPER—ELC-405

(PRACTICAL)

Full Marks : 50

Time : 3 hours

The figures in the right-hand margin indicate full marks.

(Advanced Electronics Lab)

Answer any one question selecting it by a lucky draw.

1. Design a first order low pass active filter with cut off frequency 2 KHz in PSPICE. Stimulate the circuit and plot the gain Vs. frequency curve. Also verify the cut off frequency of the plot with its given value.
2. Design an inverting amplifier circuit using OP-AMP taking input resistor $R_1 = 1\text{K}\Omega$, feedback resistor $R_2 = 6.8\text{K}\Omega$ and load resistor $R_3 = 10\text{K}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage V_{in} vs. time (t) and output voltage V_0 vs. time (t) in same graph. Also verify the gain of the amplifier with given value.

(Turn Over)

3. Design an astable multivibrator circuit with frequency 1KHz and duty cycle 66.67% using IC 555. Simulate the circuit using PSPICE and plot the output voltage *vs.* time curve. Also verify the output frequency and duty cycle of the plot with their given values.
4. Design a non-inverting amplifier circuit using OP-AMP taking input resistor $R_1 = 1 \text{ K}\Omega$, feedback resistor $R_2 = 10 \text{ K}\Omega$ and load resistor $R_3 = 10 \text{ K}\Omega$. Apply sine wave as an input signal with suitable amplitude and frequency of your choice. Simulate the circuit using PSPICE and plot the input voltage (V_{in}) *vs.* time (t) and output voltage (V_o) *vs.* time (t) in same graph. Also verify the gain of the amplifier with given value.
5. Design a second order active low pass Butterworth filter with cut-off frequency 5 KHz. Simulate the circuit using PSPICE and plot the gain *vs.* frequency curve. Also verify the cut-off frequency with the given value.
6. Design a first order high pass active filter with cut-off frequency 1 KHz in PSPICE. Simulate the circuit and plot the gain *vs.* frequency curve. Also verify the cut-off frequency from the plot with its given value.
7. Design an astable multivibrator circuit with frequency 3 KHz and duty cycle 75% using IC - 555. Simulate the circuit using PSPICE and plot the output voltage *vs.* time

curve. Also verify the output frequency and duty cycle of the plot with their given values.

8. Design a second order active high pass Butterworth filter with cut off frequency 2KHz. Simulate the circuit using PSPICE and plot the gain Vs. frequency curve. Also verify the cut-off frequency with the given value.
9. Design a differentiator circuit using OP-AMP taking input resistor $R_1 = 1 \text{ K}\Omega$, input capacitor $C_1 = 0.4 \mu\text{F}$, feedback resistor $R_2 = 8.2 \text{ K}\Omega$. and load resistor $R_3 = 10 \text{ K}\Omega$. Simulate the circuit using PSPICE and plot the transient response of the output voltage for a suitable input voltage.
10. Design an integrator circuit using OP-AMP taking input resistor $R_1 = 1 \text{ K}\Omega$ feedback resistor $R_2 = 8.2 \text{ K}\Omega$, feedback capacitor $C_2 = 0.1 \mu\text{F}$ and load resistor $R_3 = 10 \text{ K}\Omega$. Simulate the circuit using PSPICE and plot the transient response of the output voltage for a suitable input voltage.
11. Design a 3-bit synchronous MOD-5 counter using J-K flip-flop. Verify vs count sequence by LED display.
12. Design AND, OR and NOT gates using MOSFETs. Also verify their truth tables.

Marks Distribution (for PSPICE)**For Question Nos. 1 to 10 :**

	<i>Marks</i>
Theory	: 07
Circuit Design	: 10
Simulation	: 10
Verification & Accuracy	: 05
Discussion	: 03
Viva-Voce	: 10
Laboratory Note Book	: 05
Total	: 50 Marks

Marks distribution (for digital)

For Question Nos. 11 & 12 :

	<i>Marks</i>
Theory	: 05
Circuit Design	: 15
Implementation	: 07
Experimental Result	: 05
Discussion	: 03
Viva-Voce	: 10
Laboratory Note Book	: 05
Total	: 50 Marks