

2016**M.Sc.****2nd Semester Examination****ELECTRONICS****PAPER—ELC-202****Full Marks : 50****Time : 2 Hours**

The figures in the right-hand margin indicate full marks.


Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

(Digital Electronics)


Answer Q. No. 1 and any three from the rest.

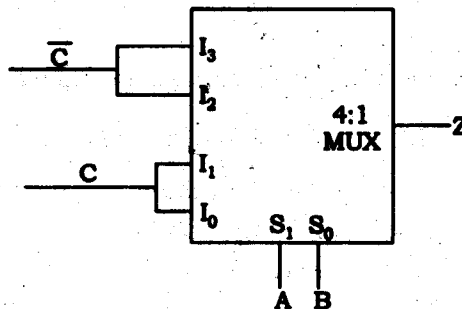1. (a) The MUX shown below is a 4×1 MUX. What is the output of the MUX?



(Turn Over)

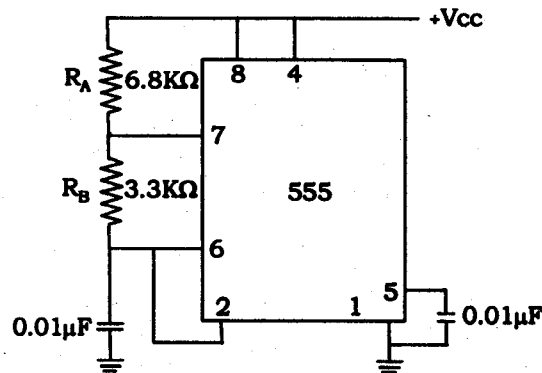- (b) What is the minimized expression for Boolean function $f(w, x, y, z) = \sum m(0, 1, 4, 5, 8, 9, 11) + dc(2, 10)$?
- (c) What is the difference between static RAM and dynamic RAM?
- (d) An 8-bit D/A converter has an output of voltage range 0 to 255V. Find the resolution of the system.
- (e) From the following figure, calculate free running frequency and duty cycle :



5×2


2. (a) Obtain the simplified expression using K-map :

$$F = ABD + \bar{A}\bar{C}\bar{D} + \bar{A}B + \bar{A}C\bar{D} + A\bar{B}D.$$

- (b) Implement the Boolean function $f = A(B + C) + DE$ using MOS transistor.

5+5

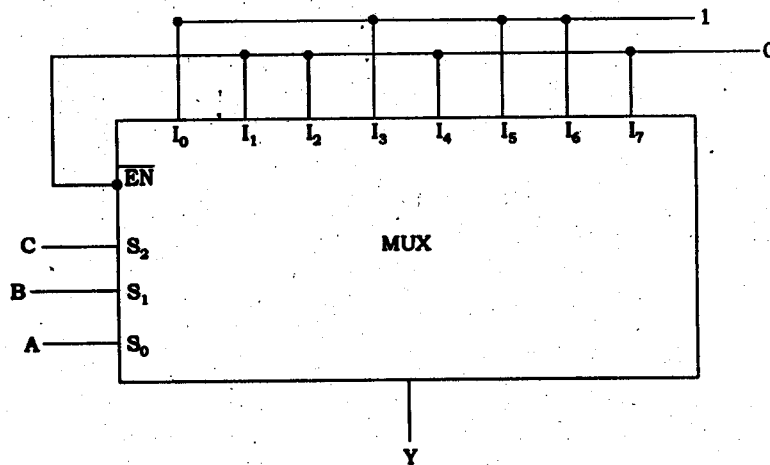3. (a) Implement NAND gate using diode and transistor only.
- (b) For the logic circuit shown below, what is its output ?



- (c) Draw the schematic diagram of an Astable multivibrator using 555 timer and explain its working principle.

2+3+(2+3)

4. (a) A 4-bit R-2R ladder type D/A converter having resistor values of $R = 10\text{k}\Omega$ and $2R = 20\text{k}\Omega$, uses V_k of 10V.

Find :

- (i) the resolution of D/A converter ;
- (ii) I_O for a digital input of 1101.

- (b) Write short note on successive approximation type A/D converter.
- (c) What is the difference between PROM and EPROM?


$$\left(1\frac{1}{2} + 1\frac{1}{2}\right) + 5 + 2$$

5. (a) Design a combinational circuit that accepts a 3-bit number as input and generates an output binary number equal to the square of the input number using ROM.
- (b) Write short note on charge coupled device.

5+5

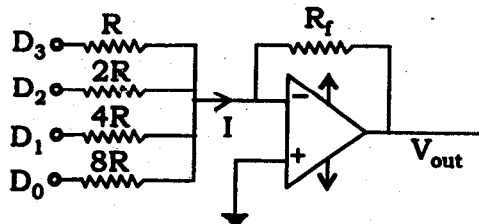6. (a) Design BCD to seven segment decoder circuit.
- (b) For a 4-bit weighted resistor DAC shown in figure below. Determine (i) the weight of each input bit if the inputs are 0V & 5V, (ii) the full scale output, if $R_f/R = 1k\Omega$.

And also the full scale output if R_f is changed to 500Ω .



$$5 + \left(1 + 1 + 1\frac{1}{2} + 1\frac{1}{2}\right)$$

[Internal Assessment — 10 Marks]