

2016

M.Sc. 2nd Seme. Examination

PHYSICS

PAPER—FHS-204

Full Marks : 40

Time : 2 Hours

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*


*Use separate Answer-scripts for Group-A & Group-B*

**Group—A**

Answer Q. No. 1 and any one from the rest.

1. Answer any *five* questions : 5×2

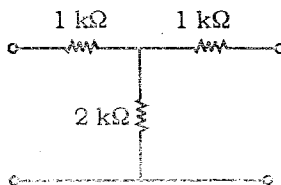(a) Convert the following T network to its  $\pi$  type.



(b) What do you mean by voltage standing wave ratio of a transmission line?

(Turn Over)

- (c) What is the origin of distortions in a transmission line ?
- (d) Write the difference between a transducer and sensor with one example for each.
- (e) Define image impedance pair of a network and find out their expressions.
- (f) Show that if a transmission line is terminated by its characteristic impedance, then there will be no reflection of the signal.
- (g) Discuss the function of a thermistor mentioning one example of it.

2. (a) What do you mean by constant-k filter ? 1

- (b) Draw the circuit diagram of a constant-k band stop filter and derive the expressions for its cut-off frequencies. Derive the expressions for attenuation constant and phase constant in the pass band and attenuation band. Also represent graphically their variations as a function of frequency in the pass band and attenuation band.

1+3+4+1

3. (a) Draw the cross sectional diagram of a triac and explain its operation by drawing its I-V characteristics.


Explain the use of a triac in a light dimmer by drawing the necessary circuit diagram and corresponding wave forms. 1+2+2

- (b) Obtain the expression of characteristic impedance and propagation constant of a transmission line with respect to its line parameters.  $2\frac{1}{2} + 2\frac{1}{2}$

## Group—B

Answer Q. No. 1 and any one from the rest.

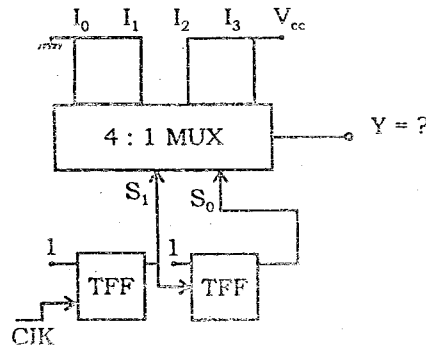1. Answer any five questions : 5×2
- Design the circuit to check whether  $A(A_1A_0)$  is greater than  $B(B_1B_0)$  or not.
  - What are the basic differences between SRAM and DRAM?
  - Explain the term "overflow" with example in signed binary arithmetics.
  - Give example of four conditional jump statements in 8085  $\mu$ p.
  - What will be the output in the following circuit for different selector inputs?



- What is the difference between natural sampling and flat-top sampling?

- (g) Show the addition and subtraction, in signed binary number representation of two numbers +9 and +5.
- (h) What are the different register present in 8085  $\mu$ p ?
2. (a) What is EPROM ? What do you mean by NVRAM ?
- (b) Show the expansion of (1k  $\times$  16) memory cell into (4k  $\times$  16) with neat diagram.
- (c) Explain briefly the structure and possible operation of A.L.U. 4+3+3
3. (a) Give the concept of D/A converter with proper circuit.
- (b) Design 1 : 4 DeMux circuit with NAND gate.
- (c) Give the meaning of the following instructions and identify the content of accumulator after execution of the programme.

```

MVI B 05
SUB A
ANA B
HLT

```

3+3+4