

**2017****M.Sc.****1st Semester Examination****ELECTRONICS****PAPER—ELC-104****Subject Code—27***Full Marks : 50**Time : 2 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*


**(Analog Electronics)**

**Answer Q. No. 1 and any three from the rest.**

1. (a) Discuss with block diagram how analog multiplication will be done using logarithmic and antilogarithmic amplifiers.
- (b) What is SMPS? What are its differences from ordinary power supply unit.


*(Turn Over)*

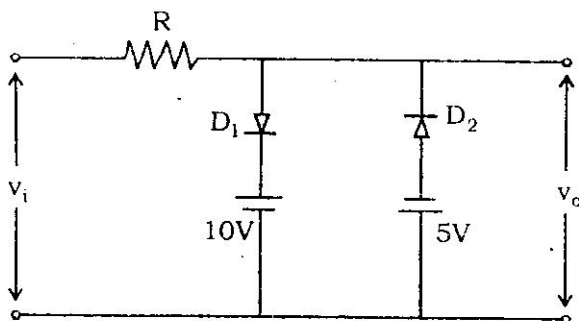- (c) Suppose a sinusoidal signal of amplitude 30V is applied as  $V_i$  in the following clipper circuit.




- (d) Construct an OR-gate with diode circuits.

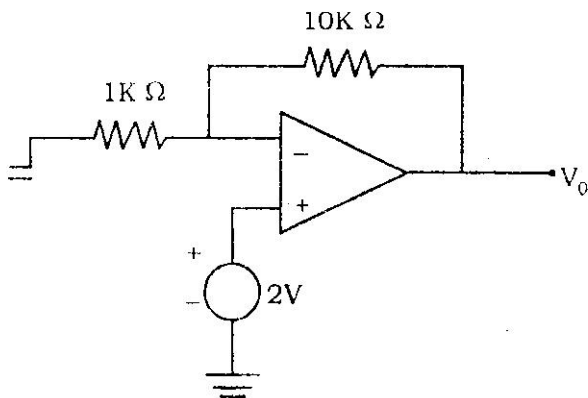- (e) Find out  $V_o$  of the following circuit.



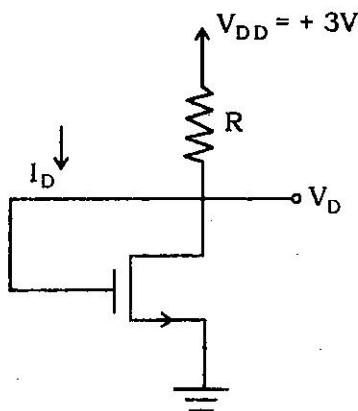2. (a) Draw the circuit diagram of an active low pass 1st order Butterworth filter and describe its principle of operation.
- (b) Define the terms Roll of rate and cut-off frequency for the above filter.
- (c) With the help of circuit diagram briefly discuss about biased clipper. 4+3+3
3. (a) How does a BJT work as an amplifier ?
- (b) Draw hybrid  $\pi$  model of BJT.
- (c) Design the circuit in following figure below to obtain a current  $I_D$  of 80rA. Find the value required for R and find the de voltage  $V_D$ . Let the NMOS transistor have  $V_t = 0.6V$ ,  $\mu_n \text{cox} = 200\mu\text{A} / \text{V}^2$ ,  $L = 0.8 \mu\text{m}$  and  $w = 4 \mu\text{m}$ . Neglect the channel length modulation effect (i.e, assume  $\lambda = 0$ )



4. (a) Explain the operation of a square wave generator using proper circuit diagram and derive the expression of its output frequency.
- (b) Draw the circuit diagram of a voltage regulator using op-amp as a comparator and explain its operation.
- 5+5
5. (a) With suitable circuit diagram explain the operation of R-C coupled amplifier. Mention function of all its component.
- (b) Write short notes on PLL.
- 5+5
6. (a) Explain Hartley oscillator with suitable circuit diagram and obtain its oscillating frequency.
- (b) Write down the principle of operation of Darlington amplifier.
- 5+5

*[ Internal Assessment — 10 Marks ]*

---