


2017**M.Sc. 2nd Semester Examination****ELECTRONICS****PAPER—ELC-203***Full Marks : 50**Time : 2 Hours**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.***(Digital Electronics and Mobile Communication)****Answer Q. No. 1 and any three from the rest.**

1. (a) What are the drawbacks of ECL logic families ?
- (b) A binary ripple counter is required to count up to 16383_{10} . How many flip-flops are required ?
- (c) What is the advantage of R-2R ladder type DAC converter over weighted resistor DAC ?

(Turn Over)

- (d) Draw the circuit of 3-input CMOS NAND gate.
- (e) What do you mean by ISDN in digital communication ?
2×5
2. (a) What is a race around condition ? How it can be avoided ?
- (b) Convert JK F/F to D F/F. (2+3)+5
3. (a) Design a type T counter that goes through states 0, 3, 5, 6, 0
- (b) Differentiate between synchronous counter and asynchronous counter.
- (c) What are the different types of shift register ? Briefly explain about them. 4+2+(1+3)
4. (a) Design Half adder logic circuit using CMOS logic.
- (b) Explain totempole arrangement in TTL logic family.
- (c) Design 4-bit odd parity generator circuit.
3+4+3

 5. (a) Design a monostable multivibrator circuit with 555 timer.
- (b) With neat circuit diagram describe the function of R-2R ladder type D/A converter. If the full scale deflection of a 4 bit D/A converter is 8 V then what is the output value at 1100?
- (c) Find out the different output state for the following circuit :



3+4+3

6. (a) What is network topology? Explain with two different such topology?
- (b) Describe briefly the idea of packet switching network.

- (c) Explain the reuse of frequency in 'cell' concept of mobile communication. With block diagram briefly demonstrate the signal transmission and reception in mobile communication. 3+3+4

[Internal Assessment — 10 marks]
