

**2017****M.Sc. 2nd Semester Examination****ELECTRONICS****PAPER—ELC-204***Full Marks : 50**Time : 2 Hours**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.***(Introduction to Electronics and  
Electronic Waste Management)****Answer Q. No. 1 and any three from the rest.**

1. (a) Sketch the CE output characteristics of a transistor and indicate active, saturation and cutoff regions.
- (b) What are the fundamental differences among class A, B, AB and C amplifiers ?
- (c) The sum and differences of two binary numbers are 1110 and 10 respectively. Find the two numbers.
- (d) Define WEEE/E - Waste.
- (e) Mention the components of E-waste management.

2×5

*(Turn Over)*

2. (a) What do you mean by rectification ? Draw the circuit diagram of a full-wave rectifier.
- (b) Explain how the dc output voltage of a full-wave rectifier is improved when a capacitor filter is used. Draw waveforms of the load voltage and diode current.

$$(2+2)+(3+1\frac{1}{2}+1\frac{1}{2})$$

3. (a) Explain the combinational and sequential circuits with examples.
- (b) Simplify the function  $X = \overline{A}BC + A\overline{B}C + \overline{A}B\overline{C}$  and draw a simplified logic circuit.
- (c) How can you implement a logic circuit that will enable any one of three switches to control a light independently of the states of the other two ?

$$(1\frac{1}{2}+1\frac{1}{2})+(2+1)+4$$

4. (a) Describe the present scenario of E-waste production.
- (b) What are the major sources of E-waste in India ? Draw a general flow diagram for the E-waste generation.

$$5+(2+3)$$

5. Write down the environmental and health implications of E-Waste.

10

6. (a) What do you mean by E-Waste management strategies ?
- (b) What was the Basel convention ? Mention the policy level initiatives in India regarding E-Waste.

$$3+(2+5)$$

[ Internal Assessment — 10 marks ]