

2017**M.Sc. 2nd Semester Examination****ELECTRONICS****PAPER—ELC-205****(Practical)***Full Marks : 50**Time : 3 Hours**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.***(Digital Electronics Lab.)***Answer one question selecting it by a lucky draw.*

- 1. Design half adder and full adder circuit using NAND gates only.**
- 2. Design half adder and full adder circuit using MUX only.**
- 3. Design half subtractor and full subtractor circuit using NAND gates only.**
- 4. Design half subtractor and full subtractor circuit using MUX only.**

(Turn Over)

5. Design 4-bit comparator circuit.
6. Design a circuit to convert a BCD to gray code and gray to BCD code.
7. Design a JK and MS flip-flop and realize its truth table.
8. Construct a MOD-10 synchronus counter.
9. Design a BCD synchronus counter.
10. Design a BCD ripple counter.
11. Design a random counter which will count following states :
(0, 3, 5, 4, 2, 6, 8, 7, 1)
12. Design a astable multivibrator using 555 timer with duty cycle. Duty cycle to be provided in the exam hall.
13. Design a R-2R ladder D/A converter.

Distribution of Marks

Theory	: 10 Marks
Circuit (Implementation)	: 10 Marks
Experiment	: 05 Marks
Results and discussion	: 10 Marks
Viva-voce	: 10 Marks
Lab. Note Book	: 05 Marks
 Total	 : 50 Marks