

2017**MCA****1st Semester Examination****BASIC ELECTRONICS & DIGITAL LAB.****PAPER—MCA-107****(Practical)***Full Marks : 100**Time : 3 Hours**The figures in the right-hand margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.*

Answer any one question.

1×70

(Lottery basis)

1. Design XOR and XNOR gates using minimum number of NAND gates.
2. Design XOR and XNOR gates using minimum number of NOR gates.
3. Design a 4 bit odd parity generator circuit.

(Turn Over)

4. Design a 4 bit even parity generator circuit.
5. Design a full adder using NAND gates.
6. Design a full subtractor using NAND gates.
7. Design a clocked SR flip-flop using NAND gates.
8. Design a J-K master slave flip-flop using NAND gates.
9. Design a circuit to convert BCD to Excess 3 code.
10. Design a 4 bit ripple counter.
11. Design a 3 to 8 line decoder using basic gates.
12. Design a full adder using 8 : 1 MUX.
13. Design a 4 bit adder using 7483.
14. Implement the following using 8 : 1 MUX
 $F(A, B, C, D) = (0, 2, 4, 6)$.
15. Design a circuit to convert Gray code to Binary number.

[Practical Note Book : 10 Marks]

[Viva-Voce : 20 Marks]
