

2015

COMPUTER SCIENCE

[ Honours ]

PAPER – II (New)

Full Marks : 100

Time : 4 hours

*The figures in the right hand margin indicate marks  
Candidates are required to give their answers in their  
own words as far as practicable*

*Illustrate the answers wherever necessary*

[ NEW SYLLABUS ]

GROUP – A

Answer any two questions : 15 × 2

1. (a) Design a synchronous counter for count the sequence 4, 6, 7, 3, 1, 4 .... avoid lockout condition use JK flip-flop. 8

(b) Design a full subtractor using demultiplexer. 7

2. (a) Prove that 5

$$\neg(P \wedge Q) \rightarrow (\neg P \vee (\neg P \vee Q)) \Leftrightarrow (\neg P \vee Q)$$

(b) Solve the recurrence relation

$$a_n = \sqrt{a_{n-1} + \sqrt{a_{n-2} + \sqrt{a_{n-3} + \sqrt{\dots}}}}$$

with  $a_0 = 4$ . 5

(c) Prove that

$n(n+1)(n+z)$  is a multiple of 6. 5

3. (a) Draw and explain the input and output characteristic of a BJT in common-emitter configuration and label the regions of operation clearly. 10

(b) What is Fermi level? Draw the fermi energy band-diagram for conductors, semi conductors and metals. 5

4. (a) What is reference model? Compare TCP and OSI models with suitable diagram? 8

- (b) What is protocol ? Explain IP addressing in details. 7

### GROUP – B

Answer any five questions : 8 × 5

5. Explain guided and unguided media. What is multiplexing. 6 + 2
6. (a) Define  $\alpha$  and  $\beta$  for transistor and also derive the relation between them. 5
- (b) What is Avalanche diode ? 3
7. How does JK FF differ from an SR FF in its basic operation ? With neat diagram explain the working of a master slave JK FF. 8
8. What is PROM ? Describe various methods which can be used to erase a PROM. Can a PROM be used to implement a truth table ? Justify your answer. 8
9. Consider the set  $A = (2, 7, 14, 28, 56, 84)$  and the relation  $a \leq b$  if and only if  $a$  divides  $b$ . Give the Hasse diagram for the poset  $(A, \leq)$ . 8

10. With neat diagram briefly explain the working of a bridge-rectifier. 8
11. Assume Message  $M = 1010101010$  bits and generator  $G = 10001$  bits. Explain, how CRC is used for error detection using above message bits and generator bits. 8
12. Write the advantages and one disadvantage of the following : 2 × 4
- (a) Hub
  - (b) Bridge
  - (c) Modem
  - (d) Switch.

GROUP – C

Answer any five questions : 4 × 5

13. What are the disadvantage of serial adder ? For which application are they preferred ? 4
14. State and prove De Morgan's theorem. 4

15. A diode whose internal resistance is  $20 \Omega$  is to supply power to a  $1 \text{ K}\Omega$  load from a  $110 \text{ V}$  (rms) source of supply. Calculate : 2 + 2
- (i) Peak load current
- (ii) DC load current.
16. Minimize the following expression : 4
- $$F(A, B, C, D) = \Pi(0, 1, 4, 5, 8, 12, 13, 14, 15)$$
17. What is bistable multivibrator ? Draw the block diagram only. 4
18. What do you mean by positive and negative feedback in amplifiers. 4
19. Draw a 4-bit parallel subtractor using full adder. 4

[ *Internal Assessment* : 10 Marks ]

---