

2015

ELECTRONICS

[**General**]

PAPER – I (New)

Full Marks : 100

Time : 3 hours

*The figures in the right hand margin indicate marks
Candidates are required to give their answers in their
own words as far as practicable*

Illustrate the answers wherever necessary

[**NEW SYLLABUS**]

GROUP – A

Answer any two questions: 15 × 2

1. (a) Draw the circuit diagram of a full-wave rectifier with a capacitor filter and explain its operation. 7

(b) Show the different current components of a $p-n-p$ transistor when its J_{EB} is forward biased and J_{CB} is reverse-biased, discussed their origin. Show the relation amongst. The different current components. 8

2. (a) With a neat sketch describe the structure of a n -channel JFET and explain its principle of operation. Why field-effect transistor is called unipolar device? 3 + 4 + 1

(b) Draw the circuit diagram of a Wien-bridge oscillator. Find an expression for frequency of oscillation. 7

3. (a) Write the characteristics of an ideal Op-Amp and a practical Op-Amp. 3

(b) Draw the circuit diagram of an adder-circuit using Op-Amp and find an expression for output voltage. 3

(c) What do you mean by class-A, class-B and class-C amplifier? Discuss their biasing conditions. 3 + 6

GROUP – B

Answer any five questions : 8 × 5

4. (a) Explain the meaning of hole as referred to a semiconductor. Is an *n*-type semiconductor negatively charged? 3
- (b) What is a *p-n* junction? Explain how does a barrier field appear across a *p-n* junction? 2 + 3
5. (a) A Sinusoidal voltage is applied to a series LCR-Circuit. Find an expression for steady state current. 5
- (b) What do you resonance condition of the above circuit? Find an expression for resonance frequency. 1 + 2
6. (a) A series RC circuit is fed with a dc source. Find an expression for charge stored in the capacitor with time. 6

- (b) What do you mean by the time-constant of the circuit? 2
7. (a) Prove that maximum power is transfer to a load when value of the load is equal to the source resistance. 4
- (b) State and explain KVL and KCL. 2 + 2
8. (a) Draw the circuit diagram of a puss-pull amplifier and explain its operation. 2 + 3
- (b) Discuss the advantages and disadvantages a class-B push-pull amplifier. 3
9. (a) Define the hybrid parameters for a basic transistor circuit in any configuration and give its hybrid model. 3 + 3
- (b) What are the advantages of h -parameters? 2
10. (a) Discuss the principle of operation of a crystal oscillator. Mention its two advantages. 5 + 1

(b) Why is the frequency stability of an oscillator high when a piezoelectric crystal is used? 2

11. (a) What do you mean by R-C coupled amplifier? Draw the circuit diagram of a R-C coupled amplifier and explain its operation. 2 + 2 + 2

(b) Also draw its frequency response characteristics and discuss it. 2

GROUP – C

Answer any five questions : 4 × 5


12. Why does electrical conductivity of a semiconductor increases with increase of temperature? What will happen, if a semiconductor is heavily-doped? 2 + 2

13. How are the width of the space-charge region and the barrier height affected when a *p-n* junction is (i) forward-biased and (ii) reverse-biased? 2 + 2

14. Explain how a Zener-diode acts as a voltage regulator. 4
15. The current flowing through a $p-n$ junction Si-diode is 60 mA for a forward bias of 0.9 volt at 300 K. Determine the static and dynamic resistance of the diode. 4
16. What is a DIAC ? Draw its current-voltage characteristic. Write its applications. 1 + 2 + 1
17. State and explain superposition theorem for network analysis. 4
18. An $n-p-n$ transistor with $\alpha = 0.98$ is operated in the CB -configuration. If the emitter current is 3 mA and the reverse saturation current is $I_{C0} = 10 \mu A$, what are the base current and the collector current ? 4

19. For inverting Op-Amp circuit (fig. below) determine input-current and output voltage for an input-voltage of 2V.

4

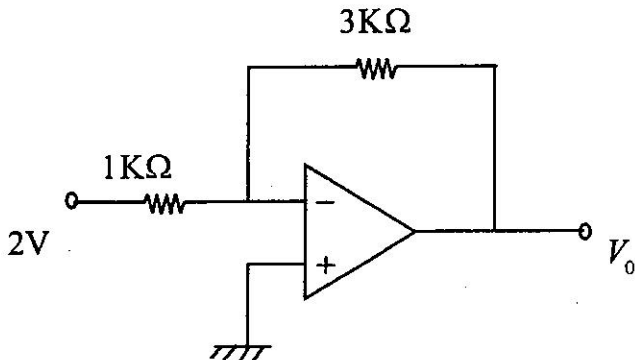

[Internal Assessment – 10 Marks]
