

**OLD**

**2015**

**Part I 3-Tier**

**ELECTRONICS**

**PAPER—I**

**(General)**

*Full Marks : 100*

*Time : 3 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

**Group—A**

Answer any two questions.

2×15

1. (a) 'The energy levels of an atom produce energy bands in a solid'. Explain. 4
- (b) What are the factors determining : (i) the width of an energy band in a crystal and (ii) the number of energy levels in the band ?

$2\frac{1}{2} \times 2$

(Turn Over)

- (c) Draw the energy-band diagram and position of Fermi level for : (i) p-type material, (ii) n-type material and (iii) unbiased p-n junction. 2×3
2. (a) How is a transistor represented as a two-port device ? 3
- (b) Define the hybrid parameters for a basic transistor circuit in any configuration and give its hybrid model. 4+2
- (c) What is Darlington connection ? Compare between an emitter follower and a Darlington pair. 3+3
3. (a) Explain the concept of feedback in amplifiers. Find out an expression for the voltage gain with feedback. 3+3
- (b) Explain under what conditions a positive feedback amplifier gives oscillations. 3
- (c) Draw the circuit diagram of a Wien-bridge oscillator with an operational amplifier as an active element. Mention the advantages and disadvantages of the Wien-bridge oscillator. 3+3

### Group—B

Answer any five questions.

5×8

4. (a) How are the width of space-charge region and the barrier height affected when a p-n junction is :  
(i) forward-biased, (ii) reverse-biased ?

$2\frac{1}{2} \times 2$

- (b) Calculate the ratio of the current for a forward bias of 0.06V to the current for the same value of reverse bias applied to a Ge p-n diode at 27°C.

3

5. (a) Draw the circuit diagram for studying the static characteristics of a p-n-p transistor operation in CE mode.

2

- (b) Sketch two important characteristics for the CE mode and explain them.

3×2

6. (a) Compare between a FET and a BJT.

4

- (b) An n-channel JEFT has  $I_{DSS} = 12\text{mA}$  and pinch-off voltage  $V_p = -4\text{V}$ . Find the drain current for  $V_{GS} = -2\text{V}$ . If the transconductance  $G_{m0}$  of a JFET with the same  $I_{DSS}$  at  $V_{GS} = 0$  is 4 millimho, find the pinch-off voltage.

2+2

7. (a) Draw a circuit diagram of a push-pull power amplifier. 3
- (b) Obtain an expression for the maximum efficiency of the circuit. 5
8. (a) Draw the structure and device symbol of a triac. 2+1
- (b) Discuss the principle of operation of triacs and name their uses. 4+2
9. (a) Find the Thevenin and Norton equivalent circuit between the terminals a, b for the network of Fig. 1 : 3+3

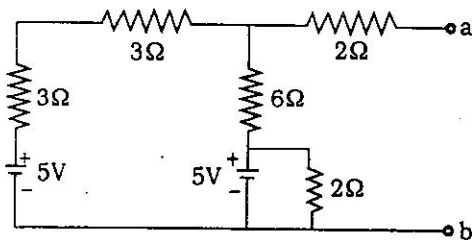


Fig. 1

- (b) Determine the resistance to be connected across a, b in Fig. 1 to dissipate maximum power and calculate the maximum power. 1+1

10. (a) A battery of voltage  $V_0$  is switched on to a series combination of a resistor  $R$  and an initially uncharged capacitor  $c$  at time  $t = 0$ . Calculate (i) the energy stored in the capacitor when it is fully charged ; (ii) the energy dissipated in the resistance during the charging of the capacitor ; (iii) the energy supplied by the battery in charging the capacitor. 2×3

- (b) What do you mean by the time constant of the circuit ? 2

11. (a) Derive expressions for voltage gain and the input impedance of an inverting amplifier using an OP AMP.

$$2\frac{1}{2} + 2\frac{1}{2}$$

- (b) Draw the circuit of voltage-to-current converter using OP AMP and explain its operation.

$$1\frac{1}{2} + 2\frac{1}{2}$$

**Group—C**Answer any *five* questions.

5×4

12. What is percentage voltage regulation? Show that for both half-wave and full-wave rectifiers, the percentage voltage regulation =  $(R_f/R_L) \times 100\%$ , where  $R_f$  is the forward resistance of a diode and  $R_L$  is the load resistance.

$$1\frac{1}{2} + 2\frac{1}{2}$$

13. Define  $\alpha$  and  $\beta$  for a transistor and obtain a relationship between them.

2+2

14. Explain different losses and leakages of a transformer.

4

15. In the circuit of Fig. 2, the switch  $K_2$  is open and the switch  $K_1$  is closed at time  $t = 0$ . At time  $t = t_0$ , the switch  $K_1$  is open and the switch  $K_2$  is simultaneously closed. Sketch the variation of the inductor current  $i$  as a function of time.

4

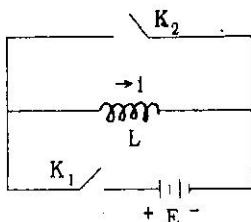


Fig. 2

16. What is the desired position of the Q-point for a minimum distortion and why? Mention the factors that affect the bias stability of a transistor. 2+2
17. Reduce the network of Fig. 3 to an equivalent T network with proper explanation. 4

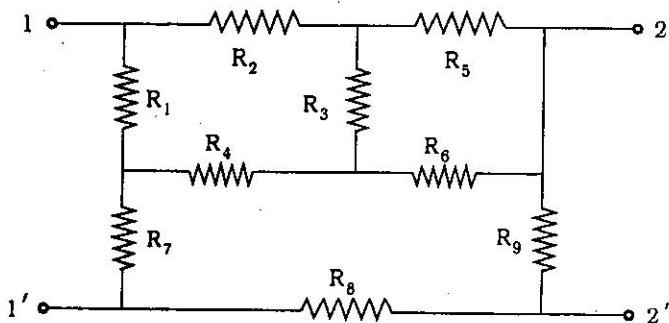


Fig. 3

18. The frequency of a Hartley oscillator is to vary from 60 - 120 KHz. The tuning capacitor can be changed from 100 - 400 pF. The transistor employed in the circuit has  $h_{fe} = 90$  and  $\Delta_{re}$  (i.e.  $h_{ie}h_{oe} - h_{fe}h_{re}$ ) = 0.2. Find the values of the inductances, neglecting the mutual inductance between them. 2+2

19. Explain the use of OP-AMP as a differentiator.

4

**[Internal Assessment — 10]**

---