

NEW
Part II 3-Tier
2015

ELECTRONICS

(Honours)

PAPER—VA

(PRACTICAL)

Full Marks : 50

Time : 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary

Answer any one question.

Group—A

(Electrical)

1. Determination of self inductance of a coil by Anderson's bridge :
 - (a) Theory and circuit diagram. 3+4
 - (b) Circuit implementation. 3
 - (c) Data for measurement of resistance of the coil (d.c. balance). 6

(Turn Over)

- (d) Data for measurement of self inductance of the coil (a.c. balance) for three capacitors. 12
- (e) Drawing of r vs. $\frac{1}{C}$ graph. 3
- (f) Calculation of self inductance. 4
2. Drawing of e-t curve, determination of thermoelectric power of a thermocouple and measurement of unknown temperature using it :
- (a) Theory and circuit diagram. 3+3
- (b) Calculation of the resistance connected in series with the potentiometer. 2
- (c) (Resistance of the potentiometer is to be supplied). Circuit implementation. 2
- (d) Data for thermo emf at five different temperatures of hot junction between 50°C and 90°C. (The cold junction is to be kept in melting ice). 13
- (e) Data for unknown temperature (specified by the examiner). 3
- (f) Drawing of e-t curve. 4
- (g) Determination of thermoelectric power at a temperature mentioned by the examiner. 3
- (h) Determination of unknown temperature. 2
3. Verification of Norton's Theorem by using a resistive Wheatstone bridge network :
- (a) Theory and circuit diagram. 3+4
- (b) Circuit implementation. 2
- (c) Measurement of load voltage (V_L) and load current (I_L) for 8 different load resistances. 8

- (d) To plot I_L against V_L and to find I_N and R_N from the plot. 4+2
- (e) Measurement of I_N and R_N from direct experiment and to compare these values with those obtained in (d). 2+2+1
- (f) To calculate the power (P_L) dissipated in the load (R_L) and to draw a graph between P_L and R_L . 3+4
4. Verification of Thevenin's Theorem by using a resistive Wheatstone bridge network :
- (a) Theory and circuit diagram. 3+3
- (b) Circuit implementation. 2
- (c) Data for load voltage (V_L) vs. load current (I_L) graph
 f o r
 8 different load resistances. 8
- (d) To plot I_L against V_L and to find I_{Th} and R_{Th} from the plot. 4+2
- (e) Measurement of I_{Th} and R_{Th} from direct experiment and to compare these values with those obtained in (d). 2+2+1
- (f) To calculate the power (P_L) dissipated in the load (R_L) and to draw a graph between P_L and R_L and to make comment on the graph. 3+4+1
5. Measurement of magnetic flux density between two pole pieces of an electromagnet by a search coil, a ballistic galvanometer and a standard solenoid (constants of search coil and standard solenoid will be supplied) :
- (a) Theory and circuit diagram. 3+3
- (b) Circuit implementation. 3
- (c) Data for I-d graph (three readings). 3

- (d) Drawing of I-d graph. 3
- (e) Ballistic throws for six different magnetizing currents of the electromagnet. 12
- (f) Calculation of B. 4
- (g) Drawing I-B graph. 4
6. To draw the resonance curve of a series L-C-R circuit, find the Q-factor of the circuit and to draw Drawing Z_L -f and $1/Z_C$ -f curves :
- (a) Theory and circuit diagram. 3+2
- (b) Circuit implementation. 2
- (c) Readings of V_R , V_L and V_C at different frequencies : (data for I-f, Z_L -f and $1/Z_C$ -f curves). 15
- (d) Drawing resonance curve (I-f curve). 4
- (e) Calculation of Q factor from resonance curve. 3
- (f) Drawing Z_L - f and $1/Z_C$ - f curves. 3+3

Marks distribution

1. Experiment (Group A) : 35 Marks
2. Laboratory Note Book : 05 Marks
3. Viva-voce : 10 Marks

Total : 50 Marks

NEW
Part II 3-Tier
2015
ELECTRONICS
(Honours)
PAPER—VB
(PRACTICAL)

Full Marks : 50

Time : 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

Answer any one question.

Group—B

(Solid State Devices and Circuits)

1. Study of a P-N junction diode :
- | | |
|---|-------|
| (a) Theory and circuit diagram. | 3+2 |
| (b) Circuit implementation on a bread board. | 2 |
| (c) Data for forward bias characteristic of the diode. | 5 |
| (d) Drawing forward bias characteristic curve. | 4 |
| (e) Determination of cut-in voltage, static resistance and dynamic resistance from the graph. | 2+3+3 |

- (f) Drawing $\ln I$ vs. V graph. 5
- (g) Determination of reverse saturation current and ideality factor from $\ln I$ vs. V graph. 3+3
2. Use of diodes in half wave rectifier circuit and bridge rectifier circuit :
- (a) Working formula for ripple factor. 2
- (b) Circuit diagrams of half wave and bridge rectifier circuits. 2+3
- (c) Implementation of the circuits on bread board. 2+2
- (d) With a suitable input A.C. signal, displaying the output waveforms from half wave and bridge rectifier circuits in a CRO monitor (to be verified by the examiner). 3+3
- (e) Determination of ripple factors of the outputs of half wave and bridge rectifiers with the help of A.C. and D.C. voltmeters. 3+3
- (f) Determination of ripple factors of the outputs of half wave and bridge rectifiers with the help of A.C. and D.C. voltmeters with a single capacitor filter in each case. 3+3
- (g) Comparison of the results of (d) to those of (e) with proper explanation. 3+3
3. Study of Zener diode :
- (a) Theory. 3
- (b) Circuit diagram and implementation of circuit on bread board for reverse bias characteristics, load regulation and line regulation. 2+2+2
- (c) Data for reverse bias characteristic of the Zener diode. 3
- (d) Drawing reverse bias characteristic curve. 3

- (e) Determination of breakdown voltage from reverse bias characteristic curve. 2
- (f) Data for Load regulation and Line regulation characteristics. 3+3
- (g) Drawing Load regulation and Line regulation characteristics. 3+3
- (h) Calculation of % of regulation for Load and Line regulations. 3+3
4. To construct a regulated power supply with a power transistor as pass element and an OPAMP as comparator :
- (a) Working formula and circuit diagram. 3+4
- (b) Calculation of components. 6
- (c) Circuit implementation on bread board (to be verified by the examiner). 6
- (d) Data for Load regulation and Line regulation characteristics. 5+5
- (e) Drawing Load regulation and Line regulation characteristics. 3+3
5. To determine the hybrid parameters of an n-p-n transistor using D.C. and A.C. sources :
- (a) Theory and circuit diagram for static output characteristics in CE configuration. 2+3
- (b) Circuit implementation for static output characteristics. 2
- (c) Data for output characteristics with specified base currents. 6
- (d) Drawing output characteristics. 6
- (e) Determination of h_{fe} and h_{oe} from output and input characteristics. 2+2

- (f) Theory and circuit diagram for determination of h_{fe} and h_{oe} with A.C. source. 2+3
- (g) Circuit implementation. 3
- (h) Determination of h_{fe} and h_{oe} . 2+2
6. To draw the characteristics of photo electric cell and to determine the stopping potential of the material of the cathode (for lights of three given frequencies of the incident light) :
- (a) Theory and circuit diagram. 3+2
- (b) Circuit implementation. 2
- (c) Photo current vs. voltage data with intensity as a parameter for three given wavelengths of incident light (for three intensities with each colour → total $3 \times 3 = 9$ curves). 16
- (d) Drawing photo current vs. voltage curves with intensity as a parameter for three given wavelengths of incident light (for three intensities with each colour → total $3 \times 3 = 9$ curves). 9
- (e) Determination of stopping potentials for the three given wavelengths. 3

Marks distribution

1. Experiment (Group B) :	35 Marks
2. Laboratory Note Book :	05 Marks
3. Viva-voce :	10 Marks
<hr/>	
Total :	50 Marks
<hr/>	