

NEW**2015****BCA****1st Semester Examination****DIGITAL ELECTRONICS****PAPER—1104***Full Marks : 70**Time : 3 Hours**The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.**Answer Q. No. 1 and any four from the rest.*

1. Answer any five questions : 5×2
- (a) What do you mean by Weighted Code ? Give example.
- (b) Convert : $(10111)_2 = (?)_{\text{Gray}}$.
- (c) Perform the following Addition of decimal numbers using BCD addition : 8 & 9.

(Turn Over)

- (d) Define Synchronous counter.
- (e) What is meant by Propagation delay in F/F?
- (f) In what condition the XOR gate acts as a Buffer.
- (g) What is clock pulse?
2. (a) What is full subtractor? Design and draw the circuit of full subtractor using only NAND gate. 5
- (b) Realize a look-ahead-carry adder. 3
- (c) Design a 3-bit binary to gray converter. 5
- (d) What is parallel adder (draw only block diagram with full adders)? 2
3. (a) Distinguish between an encoder and a decoder. 3
- (b) Draw a logic diagram for an Excess-3- to decimal decoder. Inputs and outputs should be active high. 5
- (c) Why De-Mux is called Data distributor? 2
- (d) Implement the following logic function using Mux :

$$F(A, B, C, D) = \sum m(1, 3, 4, 11, 12, 13, 14, 15).$$
 5

4. (a) How can a Decoder are used as a Demultiplexer ? 2
- (b) Implement following expression using active low decoder : 3
- $$Y = A\bar{B} + B\bar{C} + ABC$$
- (c) Design and explain octal to binary encoder. 5
- (d) Describe successive approximation method for A/D converter. 5
5. (a) Design and explain a J-K flip-flop mode by only NAND gates. 5
- (b) Convert a DFF into TFF. 4
- (c) What is race around condition ? How this condition will be removed ? 2+1
- (d) Draw MS JK FF. 3
6. (a) Design a 3-bit even synchronous counter. 5
- (b) Design a MOD-6 counter using a synchronous counter. 5
- (c) Draw and explain Serial in – Serial out (SISO) shift register. 5

7. (a) What are the difference between A/D & D/A converter? 2
- (b) Draw a AND gate using DTL.
- (c) What are the difference between DTL, TTL & ECL? 3
- (d) What do you mean by EPROM? 2
- (e) Implement $Y = A\bar{B} + ABC$ using NOR gate. 3
-