

2016

**M.Sc. Part-I Examination**

**PHYSICS**

**PAPER—IV**

Full Marks : 75

Time : 3 Hours

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

**Use separate Answerscripts for Gr. A & Gr. B.**

**Group—A**

[ Marks—40 ]

Attempt Q. No. 1, 2, 3 and any *two* from the rest.


1. Answer any *five* questions :

5×2

- (a) Define (i) loss less transmission on line and (ii) distortion less transmission line.




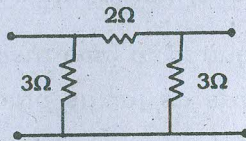- (b) In case of radio wave propagation explain the terms :  
 (i) skip distance and (ii) maximum usable frequency.
- (c) Show that the instantaneous value of an amplitude modulated wave can be represented by the sum of three waves.
- (d) Using radar range equation, explain how radar range can be increased ?
- (e) Convert the following  $\pi$ -section into its equivalent T from.



- (f) Define reflection co-efficient of a transmission line. What would be its value if a line is terminated by its characteristic impedance ?
- (g) Comment on the following terms in relation to an antenna :- (i) induction field and (ii) radiation field.
- (h) Why a photo-diode is operated in reverse bias only ?
2. Answer any *two* questions : 2×3

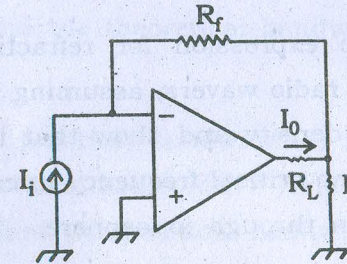- (a) Find out the expression for  $\frac{I_0}{I_i}$  in the following circuit.



- (b) A 3kW carrier signal is amplitude modulated (DSB-TC) by a single frequency sinusoidal signal. If the modulation index is 70%, determine the total power of the modulated wave. What is the power carried by the upper side band and lower side band ?
- (c) As  $V_{GS}$  is changed from  $-1V$  to  $-1.5V$  keeping  $V_{DS}$  constant,  $I_D$  of a FET drops from 7 to 5 mA. Find the transconductance of the FET. If the ac drain resistance is  $200\text{ k}\Omega$ , find the amplification factor of the given FET.

3. Answer any *one* question : 1×4

- (a) Explain the working principle of Doppler Radar.
- (b) Define the characteristic impedance  $Z_0$  of the transmission line. Deduce an expression of  $Z_0$  in terms of transmission line parameters.



4. (a) What is CMRR ? 2
- (b) Derive the expression for refractive index of ionosphere for radio waves, assuming it has a constant ionisation density and show that it is less than 1. Hence define critical frequency in case of radio wave propagation through ionosphere. 5+1
- (c) What is fading in radio waves ? 2
5. (a) Draw the circuit diagram of a constant -  $k$  high pass filter and show that it behaves as a constant -  $k$  filter. Derive the expressions for its cut-off frequency. 1+1+2
- (b) Derive the expressions for  $\alpha$ ,  $\beta$  and nominal impedance in the pass band and in the attenuation band. Also graphically show their variations as a function of frequency in the pass band and in the attenuation band. 4+2
6. (a) Define frequency modulation. Derive the expression for frequency modulated signal which is modulated by a sinusoidal modulating signal and find out its spectral components. Represent the different

frequency components in frequency domain and hence find the theoretical bandwidth of F.M.

1+1+3+1

- (b) Why the practical bandwidth of FM is not equal to the theoretical bandwidth? Write the corresponding rule to find the practical bandwidth of F.M. 2
- (c) What are the advantages of FM over AM? 2

**Group—B**


[ Marks—35 ]

Attempt Q. No. 1, 2 and any two from the rest.

1. Answer any three questions : 3×2
- (a) Distinguish between combinational logic circuit and sequential logic circuit.
- (b) What is parity generator? Mention different types of parity generators. Describe its utility.
- (c) What is the difference between RAM and SAM?
- (d) What are the different 'Flag' register in 8085  $\mu$ p?



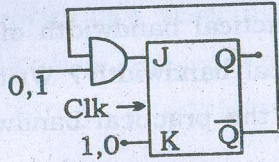(e) What will be output of the following circuit in two consecutive pulses ?



2. Answer any three bits :

3×3


(a) Explain briefly TDM-PAM.

(b) Solve the following equation by K map.

$$Y = \sum m(4, 5, 8, 10) + d(12, 13)$$

(c) Give the idea of ADC by schematic diagram.

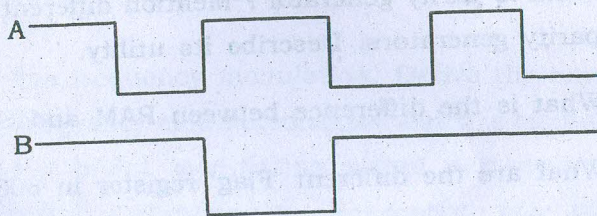(d) Draw the output of the two input Ex-NOR gate with the given inputs A and B.




(e) Write the meaning of the following instructions :  
 (i) JNZ 400F      (ii) INX H      (iii) ADI 2A.

3. (a) Design a comparator circuit which can compare  $A > B$ , where A & B are three bit binary signals.

(b) Describe the process of 4 bit PISO register with neat diagram.

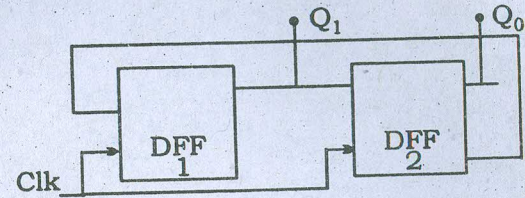(c) Explain the output state of the following circuit starting from (0, 0) initial condition.      4+4+2



4. (a) Design a decade counter and draw the output waveforms.

(b) Expand the memory capacity from  $(32 \times 4)$  to  $(128 \times 8)$  with neat diagram.

(c) Give the block diagram of PCM transmission section in digital communication system.      4+4+2



5. (a) What do you mean by mnemonics and opcode? What are the main features of 8085  $\mu$ p?
- (b) Write a short note in A.L.U.
- (c) Design Ex-nor gate memory by FPLA memory circuit.

4+4+2

