

**2018**

**M.Sc. 1st Seme. Examination**

**ELECTRONICS**

**PAPER—ELC-102**

*Full Marks : 50*

*Time : 2 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*


***Network Analysis and Synthesis***

**Group-A**

1. Answer any *four* questions : 4×2
- (a) State and explain the reciprocity theorem.

*(Turn Over)*

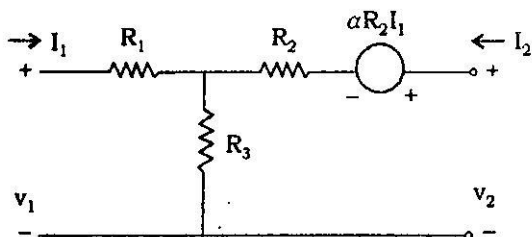- (b) Determine Z parameters of the following circuit :



- (c) Explain the following terminologies used in network graph :

(i) Branch (ii) Node (iii) Tree (iv) Loop.

- (d) Determine  $i(t)$  for the following transfer function

$$I(s) = \frac{2s + 5}{(s + 1)(s + 2)} \text{ using Laplace transform.}$$


- (e) What are the drawbacks of constant K-type filters ?

- (f) Determine the stability of the following function :

$$F(s) = (s + 1) (s + 2) (s + 3) (s + 4).$$

- (g) Explain what do you mean by critical frequencies of a driving point admittance function.

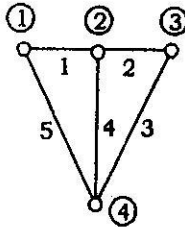- (h) The following figure represents a graph of a network. Find the trees.




**Group-B**

2. Answer any four questions :

4×4

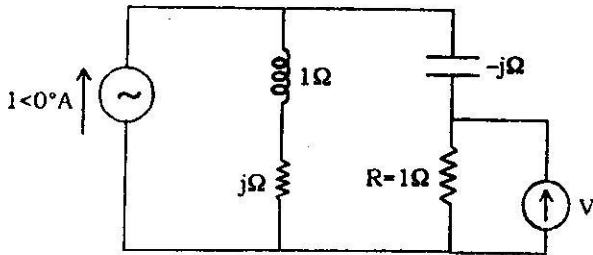- (a) In the following circuit find the reading of the voltmeter V. Interchange the current source and the voltmeter and verify the reciprocity theorem.



- (b) The reduced incidence matrix of an oriented graph is

$$A = \begin{bmatrix} 0 & -1 & 1 & 1 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Draw the graph.

(c) Explain the following types of networks :

(i) Active network,


(ii) Passive network,

(iii) Lumped and distributed networks,

(iv) Recurrent and non-recurrent networks. 1×4


(d) The Z parameters of a two port network are  $Z_{11} = 10\Omega$ ,  $Z_{22} = 15\Omega$ ,  $Z_{12} = Z_{21} = 5\Omega$ . Find the equivalent T network.

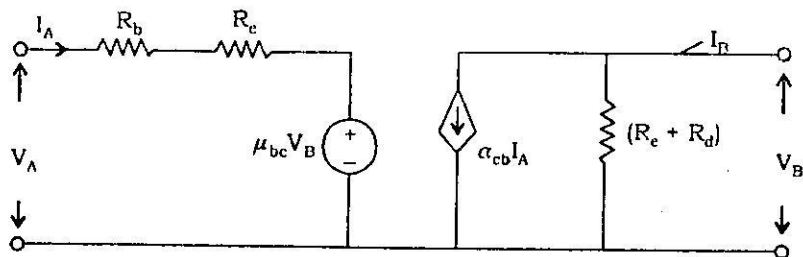(e) A common emitter transistor equivalent circuit is shown in the following figure. Find the h parameters :




(f) Prove that for a reciprocal network  $AD - BC = 1$  where A, B, C, D are the two port network parameters.

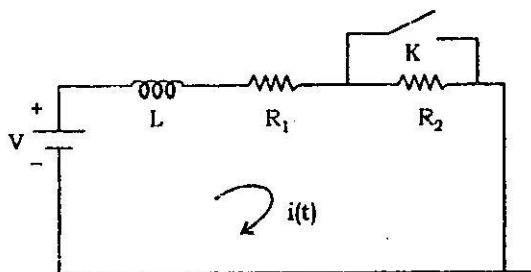(g) Consider the network shown below. Determine the current if the switch K is closed at  $t = 0$ . After the steady state has been reached determine  $i(t)$  if K is opened at  $t = 0$ .



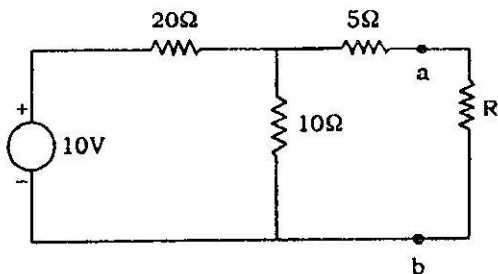- (h) Calculate the resistance  $R$  in the following circuit which will allow maximum power dissipation in it. Calculate the maximum power.




### Group-C


3. Answer any *two* questions :

2×8

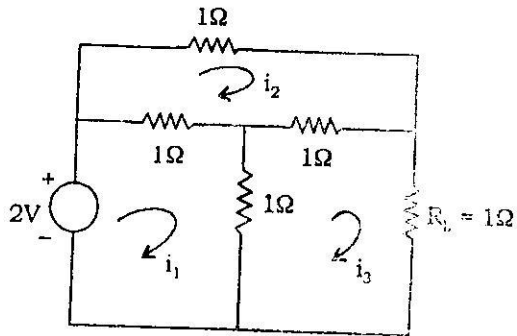- (a) (i) Apply the mesh method to find the current through the resistance  $R_L$  in the following figure :




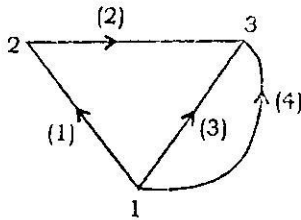- (ii) How many trees are possible for the graph shown below ?




4+4

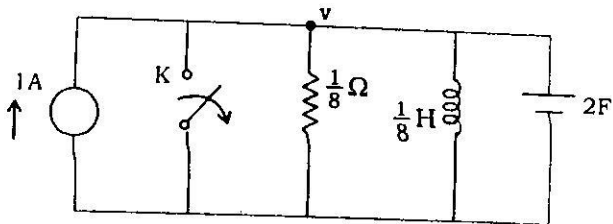- (b) (i) Determine the voltage  $V$  in the following network for  $t > 0$ , the switch  $K$  opens at  $t = 0$ .




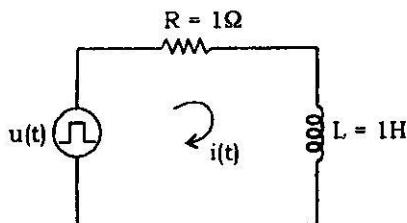- (ii) Determine the current  $i(t)$  of the following network using Laplace transform



Where  $u(t)$  is a single pulse having width  $a$ . 4+4

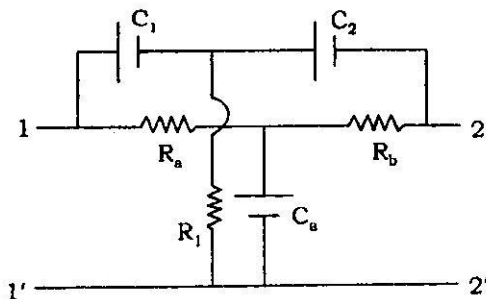- (c) (i) Determine  $y_{11}$  of the following twin-T network :



- (ii) Consider the following function and comment if such function is suitable for representing impedance function of any port

$$Z(s) = \frac{4s^4 + s^2 - 3s + 1}{s^3 + 2s^2 + 2s + 40} \quad 4+4$$

- (d) (i) A time domain voltage  $V(t)$  is applied to a series combination of RLC network. Find s domain impedance and current. Assume initial condition of the voltage in inductor to be assisting the input current and that in the capacitor opposing the input current. Draw the t-domain and s-domain circuits.
- (ii) For the given denominator polynomial of a network function, verify the stability of the network using Ruth criteria

$$Q(s) = s^4 + s^3 + 2s^2 + 2s + 12.$$

- (iii) The driving point impedance of an LC network is given by

$$Z(s) = \frac{2s^5 + 12s^3 + 16s}{s^4 + 4s^2 + 3}.$$

Determine the first cauer form of the network.

2+3+3

**Internal Assessment — 10**

---