

2018

M.Sc. 1st Seme. Examination

ELECTRONICS

PAPER—ELC-104

Full Marks : 50

Time : 2 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

Analog Electronics

Group-A

1. Answer any four questions : 4×2

(a) If the differential voltage gain and common mode voltage gain of a differential amplifier are 48 dB and 2 dB respectively, then find out its common mode rejection ratio.


(b) State and explain Miller Theorem.

(c) Describe thermal runaway of a transistor.

(d) Implement $y = \overline{AB(C + D)}$ using CMOS.

(Turn Over)

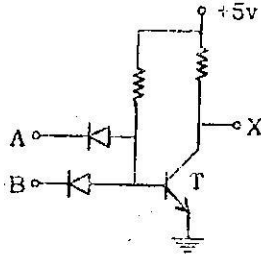(c) Identify the logic circuit shown below :



- (f) Write two advantages of crystal controlled oscillator.
 (g) Draw a voltage regulator circuit using op-amp.
 (h) Define Q point of a transistor.

Group-B

2. Answer any four questions :

4×4


- (a) By proper circuit diagram explain triangular wave generator and calculate output frequency. 3+1
 (b) Write down operating principles of PLL by using proper block diagram.
 (c) Explain the operation of a switched mode power supply with proper diagrams. Write its advantages over series regulated power supplies.
 (d) Draw the circuit diagram of a common collector transistor amplifier and explain how this can behave as an emitter follower.
 (e) How transistor works as an amplifier ? Explain it using proper VTC curve. 2+2

- (f) Show that if a MOSFET is used as a switch, its ON resistance can be expressed as

$$(r_{ds})_{ON} = \frac{1}{\mu C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_{Th})}$$

when $V_{DS} \ll (V_{GS} - V_{Th})$. The symbols have usual meanings.

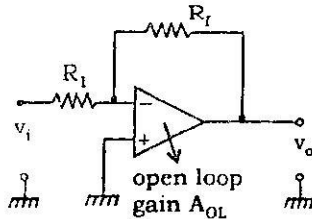
- (g) Explain series voltage regulator circuit using op-amp.
 (h) Find the expression for the voltage gain of the following inverting OP-Amp circuit :



Group-C

3. Answer any *two* questions : 2×8

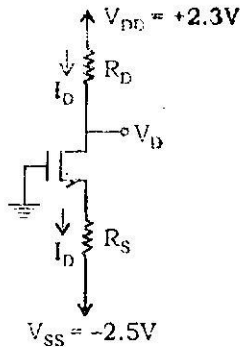- (a) (i) Explain channel length modulation of a MOSFET.
 (ii) Design the circuit of figure below, that is, determine the values of R_D and R_S so that the transistor operates at $I_D = 0.4$ mA and $V_D = +0.5$ V. The NMOS transistor has $V_t = 0.7$ V, $\mu_n c_{ox} = 100$ mA/V², $L = 1$ μ m and $W = 32$ μ m. Neglect the channel-length modulation effect (i.e., assume that $\lambda = 0$).



4+4

- (b) (i) How op-amp act as a comparator? Briefly discuss with proper circuit diagram and give input-output waveform.
- (ii) Explain Schmitt trigger circuit. (2+2)+4
- (c) Draw Common-Emitter (CE) amplifier circuit. Replace the basic circuit by its hybrid-a model. Derive input impedance, output impedance, voltage gain and current gain. 1+1+2+2+2
- (d) (i) What is an instrumentation amplifier and why this is needed? Draw the circuit diagram of an instrumentation amplifier using 3 OP-Amps and derive the expression for its output voltage in terms of input voltages.
- (ii) Explain how a current mirror circuit is realised using low- β transistors in the architecture of an OP-Amp. 5+3

Internal Assessment — 10