

2018

M.Sc. 1st Seme. Examination

ELECTRONICS

PAPER—ELC-106

(Practical)

Full Marks : 50

Time : 3 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Analog Circuit and Design Laboratory

Answer any one question selecting it by a lucky draw.

1. Use OPAMP to design a differentiation. Take a function & study its performance. Draw the transfer characteristic curve.

(Turn Over)

2. Design fixed bias transistorised amplifiers & measure V_{BE} , V_{CE} , V_{CB} , I_C , I_E at Q point

3. Use OPAMP to design an integrator. Take a function & study its performance in the circuit. Draw the transfer characteristic curve.

4. Design & study the performance of 2nd order high pass filter with following characteristics :
Cutt-off frequency :
Gain :
(To be supplied during examination).

5. Design a regulated power supply using OPAMP comparator :
Output voltage :
Current :
(To be supplied during examination).

6. Design an active low pass filter (1st order) with following specification

Cut-off frequency :

Gain :

Study the performance of the filter.

7. Design an active high pass filter (1st order) with the following specifications :

Cut-off frequency :

Gain :

Study the performance of the circuit.

8. Design a regulated power supply with following specifications :

Output voltage :

Current :

(To be supplied during examination)

9. Design and study the performance of 2nd order low pass filter with following specification :

Cut-off frequency :

Gain :

(To be supplied during examination)

Distribution of marks

Experiment	35
Viva Voce	10
Laboratory Note Book	5
<hr/>	
Total	50