

**M.Sc. 3rd Semester Examination, 2018**

**ELECTRONICS**

*(VLSI Engineering )*

PAPER – ELC-303

*Full Marks : 50*

*Time : 2 hours*

Answer Q.No.1 and any three questions from the rest

*The figures in the right hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

1. Answer the followings : 2 × 5
- (a) Draw and explain Y-chart.
  - (b) Discuss the layout design rules.
  - (c) What is a two-step diffusion process ?

*( Turn Over )*

( 2 )

- (d) Why is the choice of crystal orientation is critical for MOS devices ?
- (e) What is a MOS switch ?
2. (a) Define a class 10 clean room. If we expose a 300-mm water for 1 minute to an air stream under on laminar flow condition at 45 m/min, how many dust particles will deposit on the water in a class 10 clean room ?
- (b) Mention the different lithographic techniques used in different VLSI technology. Compare them. (2 + 2) + (2 + 4)
3. (a) What are the advantages of an ion implantation over a diffusion process ? Describe an ion implantation system with a schematic diagram.
- (b) Explain the projected range and projected straggle of ion implantation. Assume 100-KeV boron implants on a 200-mm silicon wafer at a dose of  $5 \times 10^{14}$  ions/cm<sup>2</sup>.


( 3 )

Calculate the peak concentration and required ion beam current for 1 minute of implantation.

(Given 0.31 and 0.07  $\mu\text{m}$  for projected range and projected straggle respectively)

$$(2 + 3) + (2 + 1\frac{1}{2} + 1\frac{1}{2})$$

 4. (a) What is a stick diagram? Draw a stick diagram of Fig. 1 :



( 4 )

- (b) Translate the Fig.1 into a monolithic IC clearly describing different steps.  $(2 + 2) + 6$
5. (a) Draw the two-stage CMOS OPAMP circuit and explain its working principle.
- (b) Why is compensation used in CMOS OPAMP? Draw the two-stage CMOS OPAMP circuit with compensation.  $(2 + 3) + (3 + 2)$
6. (a) Explain CMOS logic design. A logic gate has  $V_{OH} = 5V$ ,  $V_{OL} = 0.2V$ ,  $V_{IH} = 2.5V$ , and  $V_{IL} = 0.8V$ . Calculate the noise margin. (symbols have their usual meanings).
- (b) Implement the function  $F = \Sigma m(0, 1, 2, 4, 6, 8, 10, 12, 14)$  using CMOS logic.  $(3 + 2) + 5$

[Internal Assessment : 10 Marks ]

---