

**OLD**

**2017**

**Part II 3-Tier**

**ELECTRONICS**

**PAPER—II**

**(General)**

*Full Marks : 100*

*Time : 3 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**Group—A**

Answer any *two* questions.

2×15

1. (a) Convert the following to decimal numbers :
- (i)  $(30.1)_5$
  - (ii)  $(100011.0101)_2$
- (b) (i) State de Morgan's theorem and write the mathematical representation.
- (ii) Write the truth-table for an 2-input EX-OR gate.

*(Turn Over)*

(c) Simplify the following :

$$(i) f = A + B [AC + (B + \bar{C})D]$$

$$(ii) f = A [B + \bar{C}(\overline{AB + AC})] \quad (2+2)+(2+2)+(3\frac{1}{2} \times 2)$$

2. (a) Design an X-NOR gate using NOR gates.  
 (b) Implement the following equation by circuits (minimal form) :

$$y = \overline{ABCD} + \overline{AB\bar{C}D} + ABCD + \overline{ABC\bar{D}}$$

- (c) What are the differences between combinational circuit & sequential circuit?  
 (d) Design a CMOS logic NOR gate & hence explain its operation. 3+5+2+5
3. (a) Write down the truth table of SR flip-flop, its characteristic equation and then draw the circuit.  
 (b) What is race around condition? How it can be avoided.  
 (c) What is the difference between ROM & RAM? Show the design of a 4-bit RAM? (3+2+3)+2+(2+3)

**Group—B**

Answer any *five* questions. 5×8

4. Give the schematic diagram of a regulated power supply using op-amp. Explain its operation. 3+5
  
5. Give the structure and design method of a multirange DC voltmeter with 0–10 volt, 0–50 volt and 0–250 volt range.  
  
(Internal resistance of basic meter is  $100\Omega$  and full scale current is 1 mA). 4+4
  
6. (a) Explain with circuit diagram the operation of an AC voltmeter using rectifier.  
  
(b) How the R.M.S. voltage can be measured directly using a voltmeter? 5+3
  
7. Write down the principle of operation of a single phase watt-hour meter with a diagram. 5+3
  
8. Draw the block diagram of a function generator & explain its operation. 3+5
  
9. Explain with neat sketch the principle of operation of cathode ray oscilloscope. 3+5
  
10. Draw graphical representation of a saw-tooth wave. How this type of voltage wave is employed in CRO? Explain. 2+6

**Group—C**

Answer any *five* questions. 5×4

11. (a) Draw the circuit diagram of a Master-Slave flip-flop and explain its principle of operation.
  - (b) Write short note on a Q-meter. 5+3
12. Show the addition and subtraction result of the following two numbers :
 

$(10110100)_2$  and  $(01110010)_2$  2+2
13. Compare the properties of TTL & CMOS logic families. 4
14. Give the design of an opto-electronics 'XOR' gate and explain its operation. 2+2
15. What is the difference between dual beam and dual trace CRO ? 4
16. Explain Lissajous pattern of CRO. 4
17. What is the difference between edge triggered flip-flop and level triggered flip-flop ? 4
18. What is the application of MUX & flip-flop ? 4
19. What factors should be considered in choosing analog voltmeter for reporting experimental data ? 4

*Internal Assessment : 10*

---