

**NEW**

**2017**

**BCA 1st Semester Examination**

**DIGITAL ELECTRONICS**

**PAPER—1104**

*Full Marks : 70*

*Time : 3 Hours*

*The figures in the right-hand margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Illustrate the answers wherever necessary.*

Answer Q. No. 1 and any four from the rest.

1. Answer any five questions : 5×2

(a) Compare EEPROM and flash memory.

(b) Simplify the following Boolean expression into one literal

$$W' \times (Z' + YZ) + X(W+YZ).$$

(c) State De-Morgan's theorem.

*(Turn Over)*

- (d) What is edge triggered flip-flop ?
- (e) Define latch.
- (f) List out various applications of multiplexer.
- (g) What is synchronous sequential circuit ?
2. (a) Simplify the following expression using k-map method  
 $Y = \Sigma m(7, 9, 10, 11, 12)$ .
- (b) Implement AND logic using NAND gate.
- (c) Convert  $(78)_{10}$  to its binary equivalent.
- (d) What is tri-state logic ? 6+3+3+3
3. (a) Why complement is needed in computer system ?
- (b) Perform :  $(53)_{10} - (50)_{10}$  using 2's complement.
- (c) State the difference between Fan-in and Fan-out.
- (d) Draw a half-adder circuit and describe its operations. 3+3+3+6
4. (a) Represent the decimal number "27" in
- (i) BCD code
- (ii) Octal code
- (iii) Gray code.

- (b) Draw the block diagram of a digital multiplexer and explain its function.
- (c) Give the functional truth table of a 4 : 1 multiplexer and realize it using basic gates AND, OR and NOT.
- (d) Implement the expression using a multiplexer  
 $f(A, B, C, D) = \sum m(0, 2, 3, 6, 8, 9, 12, 14)$ .

3+4+4+4

5. (a) Discuss about the design of an odd parity generator.
- (b) What do you mean by race condition in flip-flop ?
- (c) Express the function  $Y = A + \bar{B}C$  in a canonical SOP form.
- (d) What is decoder ? Give a block diagram.

5+3+4+3

6. (a) Implement the Boolean function  
 $F = (A, B, C, D) = \sum m(0, 1, 3, 8, 9, 15)$  using two 4-to-1 multiplexer and one OR gate.
- (b) Explain with necessary diagram a BCD to 7 segment display decoder.
- (c) What is overflow ? Give an example.

6+6+3

7. Write short note of the following (any *three*) : 3×5

(a) Universal gates ;

(b) Decoder ;

(c) Shift Register ;

(d) Ripple counter ;

(e) Demultiplexer.

---