

2018

COMPUTER SCIENCE

[ Honours ]

PAPER –II

Full Marks : 90

Time : 4 hours

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*

GROUP – A

Answer any two questions : 15 × 2

1. (a) Prove that following is a tautology

$$A \vee (\overline{B \wedge C}) \equiv (A \vee \overline{B}) \vee \overline{C} \quad 5$$

( Turn Over )

( 2 )

(b) Solve the recurrence relation

$$a_r - 3a_{r-1} + 2a_{r-2} = 0$$

satisfying the initial condition

$$a_0 = 1 \text{ and } a_1 = 4 \quad 5$$

(c) Show that

$$\frac{1^2}{1.3} + \frac{2^2}{3.5} + \frac{n^2}{(2n-1)(2n+1)} = \frac{n(n+1)}{2(2n+1)} \quad 5$$

2. (a) Draw the circuit of two stage R-C coupled amplifier. Explain qualitatively nature of the frequency response characteristic of this amplifier. 8

(b) What is the effect on the space charge width at a *p-n*-Junction when the junction is (i) Forward biased and (ii) Reverse-biased. 7

3. (a) Describe the functions of each layers in OSI model. 7

(b) Explain the different types of ARQ techniques

( 3 )

in Data link layer with advantage and disadvantages. 8

4. (a) Explain how J-K flip-flop can be used for parallel data transfer. 5
- (b) How does a MOSFET differ from a JFET ? Sketch the structure of an  $n$ -channel depletion-type MOSFET and briefly explain its working. Draw its circuit symbol. 1 + 4 + 1
- (c) Design a logic circuit to implement binary to excess -3 code converter. 4

#### GROUP – B

Answer any five questions : 8 × 5

5. Using 4 bit parallel binary adder, design a circuit to perform BCD addition. Show different condition with different examples. 8
6. (a) What is meant by Common-Mode Rejection Ratio (CMRR) of an op-amp ? 2
- (b) Explain the concept of virtual ground in

connection with op-amp. Draw the circuit diagram of a difference amplifier using op-amp and find an expression for the output voltage. 2 + 4

7. (a) Define conjunctive canonical form and disjunctive canonical form. 1 + 1
- (b) What is the major restriction while operating a pulse triggered flip-flop ? 2
- (c) An 8-to-1 Mux has inputs a, b, c connected to the selection inputs. The data inputs  $d_0$  to  $d_7$  are as follows  $d_1 = d_2 = d_7 = 0$ ,  $d_3 = d_5 = 1$ ,  $d_0 = d_4 = d$  and  $d_6 = d'$ . Determine the Boolean expression that mux implements. 4
8. Explain HDLC frame format and how explain the concept of piggybacking used using HDLC frame during transmission. 8
9. Explain different types of switching techniques in brief. Compare and contrast between circuit switching and virtual circuits. 8

10. Write down the characteristics of zener diode.  
Describe the phenomenon of zener breakdown. 8

11. Reduce the expression using k-map and implement  
through minimum universal gates

$$f = \Pi M(2, 7, 9, 10, 11, 12, 14, 15) \\ + d(0, 4, 6, 8) \quad 8$$

12. (a) Draw a block diagram of an 8 : 1 MUX.  
Design an 8 : 1 MUX using two 4 : 1 MUX  
and one 2 : 1 MUX. 4

(b) Draw the function

$$F(D, C, B, A) = \Sigma m(0, 5, 7, 9, 10, 11, 13, 15) \\ \text{using } 8 : 1 \text{ MUX.} \quad 4$$

### GROUP – C

Answer any five questions : 4 × 5

13. What is bit stuffing and de-stuffing explain with  
example. 4

14. State and prove De Morgan's Law. 4

15. What is Router ? Differentiate function of Router, Switch and Hub. 4
16. Using set theory solve the following : 4  
Among the first 500 positiver integers
- (a) Determine the no of integers which are not divisible by 2, nor by 3, nor by 5.
- (b) Determine the no of integers which are exactly divisible by one of them.
17. Define set and power set with example. 4
18. Write down the character of tri-state buffer. 4
19. A combinational circuit is defined by the following three functions :
- $$f(x, y, z) = x'y' + xyz'$$
- $$g(x, y, z) = x' + y \text{ and}$$
- $$h(x, y, z) = xy + x'y'$$
- Design the circuit with a decoder and external gates. 4

20. Fibonacci series can be described as 1, 1, 2, 3, 5, 8, .....  $\alpha$  Formulate a recurrence relation defined on it. Hence solve that Recurrence relation for eliminating recursion using Generating Function. 4
-