

M.Sc. 1st Semester Examination, 2019

ELECTRONICS

(Network Analysis and Synthesis)

PAPER – ELC-102

Full Marks : 50

Time : 2 hours

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary


1. Answer any *four* questions : 2 × 4
- (a) State and explain the superposition theorem. 2
- (b) What do you mean by critical frequencies of a driving point admittance function ? 2
- (c) Write down the drawbacks of constant-*k* type filters. 2
- (d) Explain the significance of the Pole-Zero plot of a network function. 2

(e) Express the function

$$F(s) = \frac{(s+2)}{(s+1)^2}$$

in a partial fraction expansion. 2

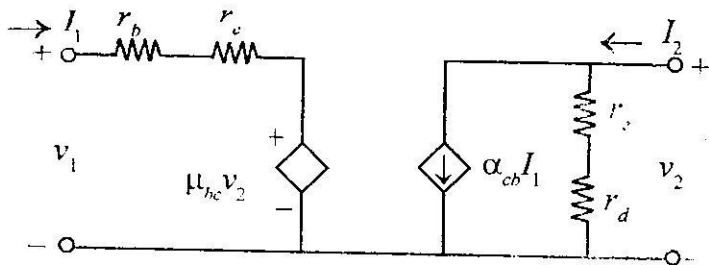(f) Find out the h -parameters of the following circuit. 2



(g) Comment of the following function $Z(s)$ could be an impedance function or not? 2


$$Z(s) = \frac{15(s^3 + 2s^2 + 3s + 2)}{s^4 + 6s^3 + 8s^2}$$

(h) If the reduced incidence matrix of a network


$[A] = \begin{bmatrix} 1 & 0 & -1 & 1 \\ -1 & 1 & 0 & 0 \end{bmatrix}$. How many trees are possible? 2

2. Answer any *four* questions : 4 × 4

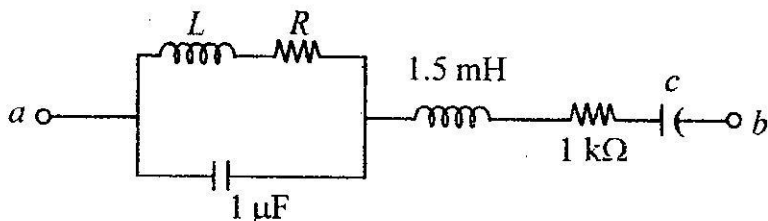
- (a) The following network is to have a pure resistance of $11\text{k}\Omega$ across the terminal a and b at a frequency of 10 kHz . Determine the values of R , L , and C . 4



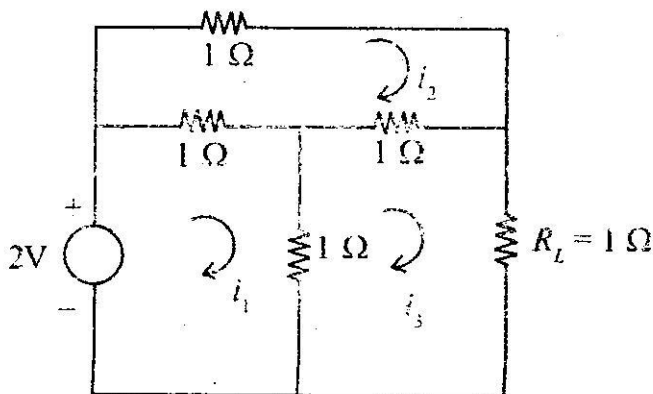
- (b) Apply the mesh methods to find out the current through resistance R_L . 4



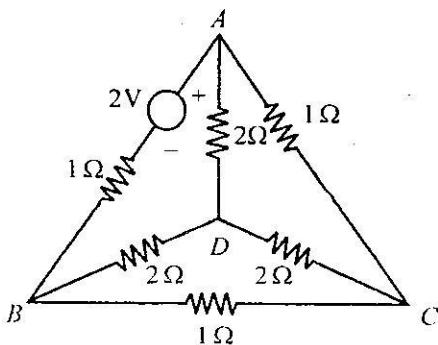- (c) For the following network, write down the tie-set matrix and determine the KVL equations. Also calculate the loop currents. 4



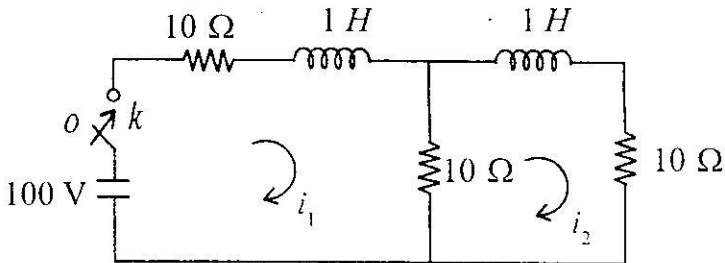- (d) Prove that for a reciprocal network $AD - BC = 1$. 4
- (e) Using Laplace transform determine $i_2(t)$ in the following circuit when switch k is closed at $t = 0$. 4




- (f) Calculate the values of the shunt and the series elements of a high pass π -section filter having a cut-off frequency of 10 kHz. The nominal resistance of the filter is 500Ω . 4

- (g) For the given denominator polynomial of a network function, verify the stability of the network using R-H criteria


$$Q(s) = s^4 + s^3 + 2s^2 + 2s + 12 \quad 4$$

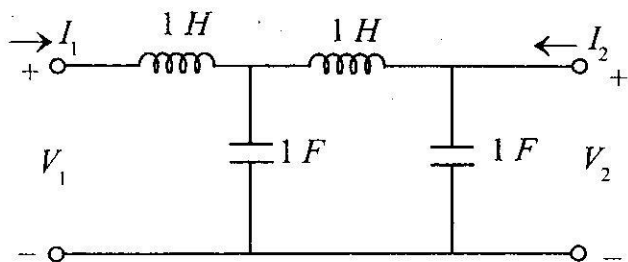- (h) Find out the input impedance of the following network. 4



3. Answer any *two* questions : 8 × 2

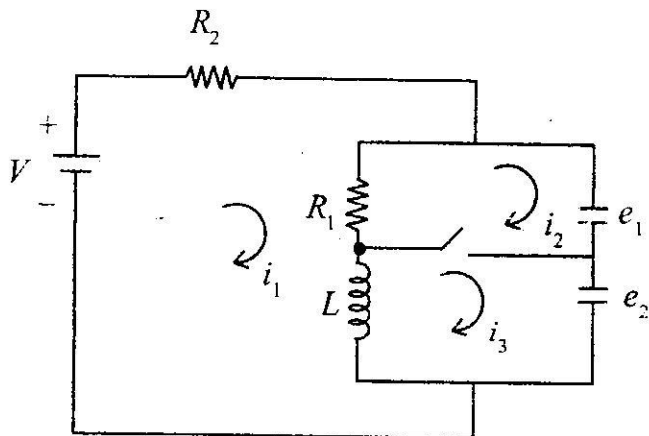- (a) (i) Determine $i_1(0+)$, $i_2(0+)$ and $i_3(0+)$ of the following circuit.



- (ii) Let us consider two Network N_a and N_b are in parallel connection. The y -parameters of network N_a and N_b are

$$\begin{bmatrix} y_{11a} & y_{12a} \\ y_{21a} & y_{22a} \end{bmatrix} \quad \text{and} \quad \begin{bmatrix} y_{11b} & y_{12b} \\ y_{21b} & y_{22b} \end{bmatrix}$$


respectively.

Prove that the y -parameters of the combined network


$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} y_{11a} + y_{11b} & y_{12a} + y_{12b} \\ y_{21a} + y_{21b} & y_{22a} + y_{22b} \end{bmatrix}$$

4 + 4

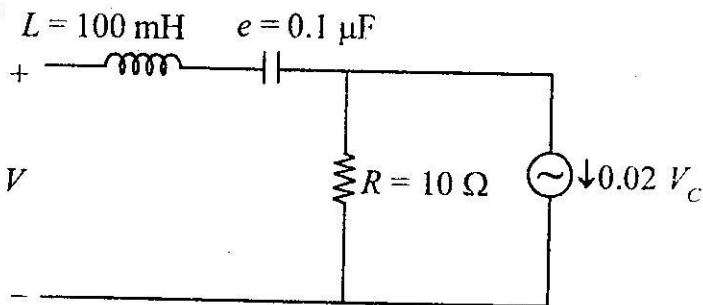
- (b) (i) Determine the resonant frequency, Q -factor at resonance and bandwidth of the following circuit.



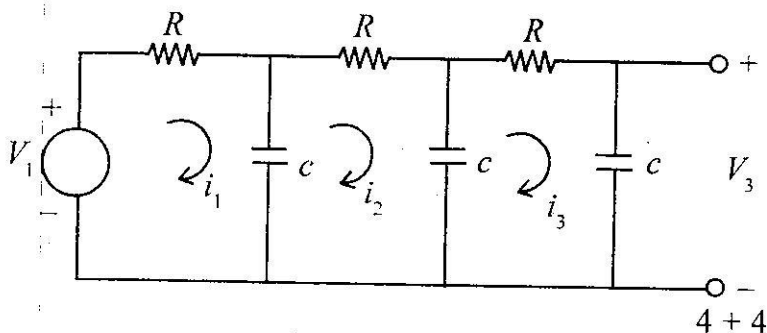
- (ii) Find the ratio of the voltage v_3 to the voltage v_1 , when phase difference between v_1 and v_3 is 180°



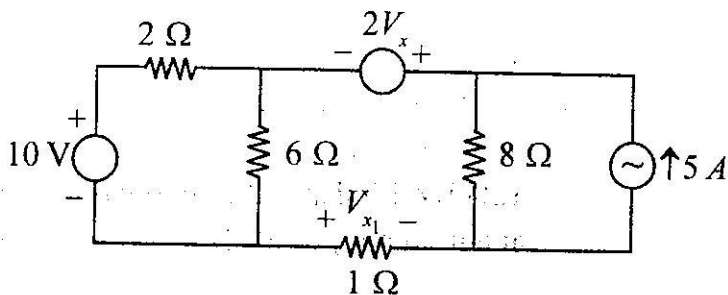- (c) (i) Use principle of superposition to find the current I in the following circuit.




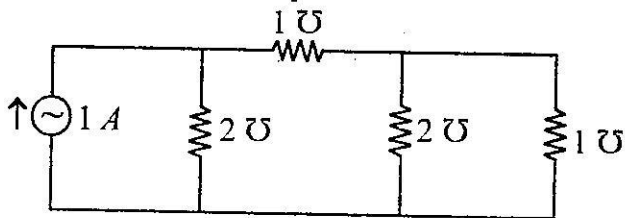- (ii) For the following network determine fundamental cut-set matrix and hence find the KCL equation.



4 + 4

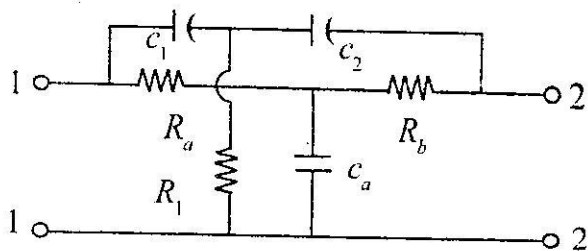- (d) (i) Determine y_{11} of the following Twin-T network.



- (ii) Design a constant- K low pass T-section filter with nominal resistance of 50Ω to produce cut-off at a frequency of 1.2 kHz . Find also the attenuation in dB at a frequency of 2 kHz . 4 + 4

[*Internal Assessment* : 10 Marks]
