

2019

MSc

2nd Semester Examination

ELECTRONICS

PAPER – ELC-203

Full Marks: 50

Time: 2 Hours

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their


Own words as far as practicable.

Illustrate the answers wherever necessary.

1. Answer any **04** questions out of **08** Questions.

2x4

 - i) Why is ECL called the fastest of all logic families?
- ii) Implement the following function with a MUX: $F(a, b, c) = \sum m(1, 3, 5, 6)$ choose a and b as select inputs.
- iii) The J-K FF shown below is initially cleared and then clocked for 5 pulses, the sequence at the Q output will be.



- (A) 010000
 (B) 011001
 (C) 010010
 (D) 010101

- iv) Implement the logic expression $Y = AB(C+DE)$ using CMOS logic.
- v) Find out the output voltage when input is 0100 using 4 bit R – 2R ladder type ADC.
- vi) Differentiate between static and dynamic memory.
- vii) A binary channel with bit rate $r_b = 36000$ bits per second (b/s) is available for PCM voice transmission. Evaluate the approximate values of the sampling rate f_s , the quantizing level q and the number q binary digits v . Assume $f_m = 3.2$ kHz.
- viii) Write down advantages of PCM system over other communication system.

2. Answer any **04** questions out of **08** questions.

4×4

- i) Write short note on successive approximation type A/D converter.
- ii) Design Ring counter, mention its different states.
- iii) Convert SR to JK F/F.
- iv) Design 2 – bit magnitude comparator.
- v) Design of a 4 bit Binary to gray code converter.
- vi) Reduce using mapping the expression $f = \sum m (0, 1, 2, 3, 5, 7, 8, 9, 10, 12, 13)$ and implement the real minimal expression in universal logic.
- vii) A television signal having a bandwidth of 4.2 MHz is transmitted using binary PCM system. Given that the number of quantization level is 512. Determine.
 - 1) Code word length
 - 2) Transmission bandwidth
 - 3) Final bit rate
 - 4) Output signal to quantization noise ratio.
- viii) With the help of block diagram describe PCM generator.

3. Answer any **02** questions out of **04** questions.

2×8

- i) Design of a synchronous BCD counter using J – K Flip – flops.

- ii) With the help of proper circuit diagram explain the operation of monostable multivibrator.

- iii) Explain the operation of two input TTL NAND gate.

- iv) a) Design a combinational circuit that accepts a 3 – bit number as input and generates an output binary number equal to the sequence of the input number using ROM.
b) Write short notes on change – coupled device.

(Internal assessment - 10 marks)