

2012**MCA****1st Semester Examination****BASIC ELECTRONICS & DIGITAL LOGIC****PAPER—MCA-103**

Full Marks : 100

Time : 3 Hours


*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Illustrate the answers wherever necessary.*

Answer any seven questions.

1. (a) What are intrinsic and extrinsic semiconductors? What are p-type and n-type crystals? Is an n-type semiconductor negatively charged? 2+2+1
- (b) What is static resistance & what is dynamic resistance? 2
- (c) Draw the practical volt-ampere characteristics of Ge-diodes and Si-diodes showing the cut in voltages. 3

2. (a) Establish the relation $I_c = \beta I_B + (1 + \beta) I_{CBO}$ for CE configuration in active region. 2
- (b) A transistor with $\alpha = 0.98$ is operated in CB configuraton. If the emitter current is 3 mA and the reverse saturation current is $I_{CO} = 10\mu A$, what are the base current and the collector current? 3
- (c) Draw the output characteristic curves of an n-p-n transistor in CE mode. Discuss about the different operating regions. 5
3. (a) What is Thermal runaway? 2
- (b) Define JFET parameters and give the relation between them. 5
- (c) Write the difference between FET and BJT. 3
4. (a) What is OP-AMP? Define CMRR & slew rate. 1+2+2
- (b) Derive the expression for the OPAMP used as an adder and draw the circuit diagram. 3+2
5. (a) What do you mean by faithful amplification? 2
- (b) Draw and briefly explain the circuit diagram of an emitter bias. 4

 - (c) The circuit of a base resistor biased transistor is given below : 5



- (i) Draw the DC load line. 2
- (ii) Calculate the operating point. 2
6. (a) Simplify Boolean function $xz + x'yz$ to a minimum number of literals. 2
- (b) Use only NOR gates to design a clocked S-R flip-flop. What is forbidden state? 4+2
- (c) Show that the dual of the exclusive - OR is equal to its complement. 2

7. (a) Design full subtractor using 4 : 1 Multiplexer. 5
 (b) Write short notes on Octal to binary encoder. 3
 (c) What is parity bit generator? 2
8. (a) Draw and explain working principle of clocked master-slave JK flip-flop using NAND gates only. 4
 (b) What is the basic difference between a D flip-flop and a T flip-flop? 2
 (c) Use only NAND gates to design a clocked S-R flip-flop and show its truth table. 4
9. (a) What is universal shift register? Design it. 6
 (b) What are the advantages and disadvantages of ripple counter? 2
 (c) What is the modulus of a counter? 2
10. (a) Design 3 bit synchronous down counter. 5
 (b) Design XOR gate using NAND gates. 2
 (c) What is the difference between EPROM and EAROM? 3

[Internal Assessment — 30]
