

2019

COMPUTER SCIENCE

[Honours]

PAPER – II

Full Marks : 90

Time : 4 hours

*The figures in the right hand margin indicate marks
Candidates are required to give their answers in their
own words as far as practicable*

Illustrate the answers wherever necessary

GROUP – A

Answer any two questions : 15 × 2

1. (a) Draw and describe Master-Slave JK flip-flop using NAND Gate. 6

(b) Prove that : 4

$$(A + B)(\overline{A\overline{C}} + C)(\overline{\overline{B} + AC}) = \overline{A}B.$$

(c) What is meant by edge triggering ? Give the difference between positive edge triggering and negative edge triggering. 2 + 3

2. (a) Prove that : 5

$$\neg(P \wedge Q) \rightarrow (\neg P \vee (\neg P \vee Q)) \leftrightarrow (\neg P \vee Q)$$

(b) Solve the recurrence relation

$$a_n = \sqrt{a_{n-1} + \sqrt{a_{n-2} + \sqrt{a_{n-3} + \sqrt{\dots}}}}$$

with $a_0 = 4$. 5

(c) Prove that
 $n(n+1)(n+2)$ is multiple of 6. 5

3. (a) What is IP Address ? Discuss about the structure of class C IP address format. 5

(b) With a neat diagram draw and explain the basic structure of n -channel JFET. 5

- (c) Draw and describe the four bit comparator circuit. 5
4. (a) What is reference model ? Compare TCP and OSI models with suitable diagram. 8
- (b) What is Fermi level ? Draw the fermi energy band-diagram for conductors, semi-conductors and metals. 7

GROUP – B

Answer any five questions : 8 × 5

5. Explain guided and unguided media. What is multiplexing ? 6 + 2
6. Explain the operation of a bi-directional shift register. 8
7. Use Boolean algebra to simplify the following Boolean expression and implement in NAND logic. 8
- $f(A, B, C, D) = \sum m(10, 11, 14, 15)$

8. (a) Design of MOD-10 counter. 6
(b) What do you mean by positive logic and negative logic. 2
9. Write down the different characteristics of Zener diode. Describe the phenomenon of Zener breakdown. 6 + 2
10. Design an 16 : 1 MUX using 4 : 1 MUX and necessary gates ? 8
11. Assume Message $M = 1010101010$ bits and generator $G = 10001$ bits. Explain, how CRC is used for error detection using above message bits and generator bits. 8
12. Write the advantages and disadvantages of the following : 2×4
(a) Hub
(b) Bridge
(c) Modem
(d) Switch.

GROUP – C

Answer any five questions : 4 × 5

13. What is network topology ? Briefly explain it. 4
14. Write a short note on seven segment display. 4
15. Explain the working principle of 1:16 demultiplexer. 4
16. Draw a 4-bit parallel subtractor using full adder. 4
17. Draw HDLC frame structure. 4
18. Write down the characteristics of tri-state buffer. 4
19. What is congestion ? How does it occurs ? 4
20. Describe Nyquist Bit Rate and Shannon capacity of a channel. 2 + 2

[*Internal Assessment : 10 Marks*]
