

**2019**  
**Part – II**  
**COMPUTER SCIENCE**  
**(Honours)**  
**Paper – V**  
**(Practical)**  
**(Set – I)**

*Full Marks – 50*

*Time : 4 Hours*

*The figures in the right-hand margin indicate marks.  
Candidates are required to give their answers in  
their own words as far as practicable.*

**Unit – II**  
**GROUP – A**

**[Digital Electronics]**

20×1

1. Design a circuit that implements 3-bit X-OR and 3-bit X-NOR gate. Show their outputs.
2. Design a 1×8 De - MUX using NAND gats.

**P.T.O.**

3. Implement  $F = ABC + A\bar{B}C + AB\bar{C} + \bar{A}B\bar{C}$  using NOR gates only.
4. Design a code converter circuit that convert a 4-bit number to its equivalent Gray code.
5. Design a J-K flip flop using NAND gates.
6. Design a D flip flop using NOR gates.
7. Design a MOD -8 counter using J-K flip/flops.
8. Design a 4-bit circular right shift register.
9. Design a 2-bit magnitude comparator circuit.
10. Design a full adder circuit using logic gates.

## GROUP – B

### [Microprocessor & Interfacing]

#### Microprocessor

12×1

1. Write an 8085 ALP to find maximum of three numbers.
2. Write an 8085 ALP to sort three number present in  $F000_H - F002_H$  in ascending order.
3. Write an 8085 ALP to find number of 0,s in c-register.

4. Write an 8085 ALP to count number of even numbers among the 8-bit numbers present in memory locations  $D000_H - D0009_H$  .
5. Write an 8085 ALP to move a memory block from  $DA00_H - DA13_H$  to  $DA20_H - DA33_H$  .
6. Write an 8085 ALP to find Excess – 3 code of the 8-bit number present in memory location  $F000_H$ .
7. Write an 8085 ALP to increment all the memory contents in memory location range  $F200_H - F210_H$ .
8. Write an 8085 ALP to display 0 – 9 after a gap of roughly 1 second time.

#### Interfacing with 8255

8×1=8

1. Write an 8085 ALP to display "100."
2. Write an 8085 ALP to display "DEER".
3. Write an 8085 ALP to display "hello".
4. Write an 8085 ALP to generate a square wave and display it.

Viva-voce : 5 Marks

Practical Note Book : 5 Marks

---