

2008

ELECTRONICS

[1st Semester]

PAPER—EL-1103

Full Marks : 50

Time : 2 hours

Answer Q. No. 1 and any three from the rest

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

[University written examination—40 Marks
Internal Assessment—10 Marks]

1. Answer *all* questions: 2 × 5

(a) What do you mean by the characteristic impedance of a network?

(b) Obtain the Laplace transform of $e^{-at} \sin \omega t$.

(Turn Over)

(c) The system function of a network is given by

$$H(s) = \frac{(s + 2)(s + 5)}{s + 1}$$

Test whether it is a positive real function or not.

(d) What do you mean by resonance? Define Q factor in a series LCR circuit.

(e) Distinguish between active and passive filters.

2. (a) Draw the pole-zero diagram of the system function

$$H(s) = \frac{s(s + 3)}{(s + 1)(s^2 + 4s + 13)}$$

(b) For the circuit as shown in Fig. Q. 2 (b), find the current I using superposition theorem.

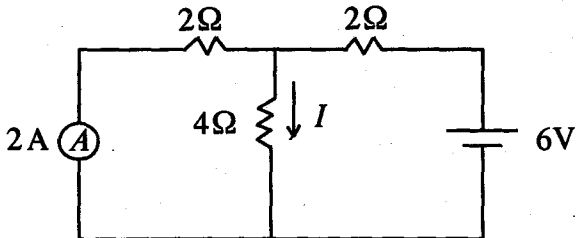


Fig. Q. 2 (b)

5 + 5

3. (a) Derive an expression for the cut-off frequency of a constant k -high-pass filter.
- (b) Design a T and π section constant k -high pass filter having cut-off frequency 10 kHz, and design impedance (R_0) is 500 Ω . Also find
 (i) its characteristic impedance at 25 kHz
 (ii) attenuation at 6 kHz. 4 + (4 + 1 + 1)
4. (a) Write down the necessary condition of stability of a network function [$F(s)$].
- (b) The driving point impedance of a LC network is given by

$$Z(s) = \frac{6s^3 + 2s}{12s^4 + 8s^2 + 1}$$

Develop the Cauer first form network for given function.

- (c) What do you mean by Bode diagram? 3 + 5 + 2
5. (a) Write down the difference between 'Band-pass' and 'Band-stop' filters.

- (b) A simple RC low pass filter is to be design that the output voltage be attenuated at 3 dB. at 50 Hz. Calculate the time constant and the suitable values of R and C .
- (c) Calculate the upper and lower cut-off frequencies and voltage amplification between these two frequencies for a band-pass active filter.

Given: $R_1 = R_2 = 10 \text{ k}\Omega$

$$R_{f1} = R_{f2} = 100 \text{ k}\Omega$$

$$R_L = R_H = 10 \text{ k}\Omega$$

$$C_L = 1\mu\text{F}, C_H = 1\text{pF} .$$

2 + 4 + 4

6. (a) What are the condition of a polynomial is said to be Hurwitz?

(b) Check whether the following polynomial are Hurwitz:

$$P(s) = s^5 + s^3 + 5.$$

(c) Find the second Foster form of the driving point admittance function

$$Y(s) = \frac{s(s^2 + 4)}{2(s^2 + 1)(s^2 + 9)}$$

2+3+5