

2007**ELECTRONICS****PAPER-II***Full Marks : 75**Time : 3 hours**The figures in the right-hand margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.**Write the answers questions of each Group in separate books.**Answer Q. No. 1 and any three from the rest in each group.***Group - A***(Marks : 40)*

- (a). **Define** V.S.W.R, Give the relation between V.S.W.R and reflection coefficient: 2
- (b) **What do you mean by Phase constant of a transmission line?** 2
- (c) **Define the directivity of an antenna.** 2
- (d) **What do you mean by Skip distance ?** 2
- (e) **What do you mean by cut-off wave length in a rectangular wave guide.** 2
- (a) **Derive the general solutions for the line voltage and line current in terms of the distance variable d in the sinusoidal steady state.**
- (b) **Discuss the reasons for transmission-line matching and the principle behind matching.** (3+3)+(2+2)

3. (a) When is it meaningful to attribute a group velocity to a signal comprised of more than two frequencies ? Why?
- (b) Briefly outline the procedure for deriving the expressions for TM mode fields in a rectangular waveguide.
- (c) Why is the dimension b of a rectangular waveguide generally chosen to be less than or equal to one-half the dimension a ? (1+2)+5+2
4. (a) To what does the word 'retarded' in the terminology 'retarded magnetic vector potential' refer? Explain.
- (b) Why microwave region is called a transition region ? Deduce an expression for field distribution across the aperture of a parabolic reflector . (1+2)+(2+5)
5. (a) Explain the phenomenon of selective fading in communication through tropospheric waves. What is duct propagation ?
- (b) Show that the phase velocity of a plane electromagnetic wave propagating in an ionized medium is greater than the velocity of light in free space.
- (c) Obtain the relationship between the maximum radio frequency reflected from an ionospheric layer to the corresponding critical frequency . (2+2)+3+3
6. Write short notes (any two) 5x2
- (a) Characteristics of Plasma.
- (b) MUF.
- (c) Resonant and non-resonant antenna.
- (d) Excitation of modes in waveguides.

Group - B

(Marks 35)

1. (a) State Superposition theorem.
- (b) Distinguish between active and passive filters.
- (c) Draw the circuit diagram of a band stop filter.
- (d) What do you mean by image impedance of a network.
- (e) Draw two different kinds of waveform possessing odd symmetry. 1X5

2. (a) For the network as shown in Fig Q. 2(a), find the current I using superposition theorem. 5

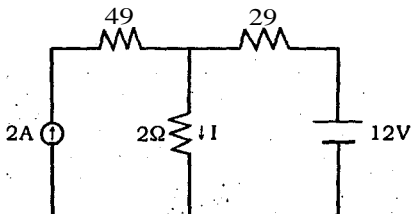


Fig Q. - 2(a)

- (b) For the a. c. circuit as shown in Fig Q. 2(b), find I , I_x and I_c in phasor form.

Given : $v(t) = 220J \sin 314t$

5

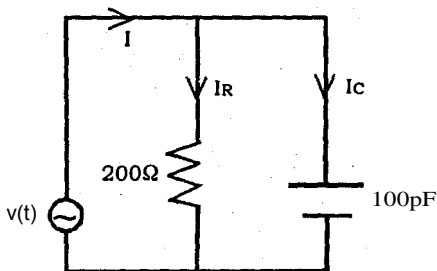


Fig Q. 2(b)

3. (a) Draw Pole-zero diagram of the system function

$$Z(s) = \frac{s(s+3)}{(s+1)(s^2+4s+13)}$$

5

(b) Following data were obtained experimentally for an unknown two-port network. Compute the Z-parameters. 5

	V1	V2	I1	I2
Output open	100V	60V	10A	0
Input open	30V	40V	0	3A

4. (a) A system has a system function given by

$$H(s) = \frac{X(s)}{(s+1)(s+3)}$$

Given $x(t) = \cos t$.

Determine $y(t)$ using Laplace Transform. 5

- (b) (i) Obtain the expression for gain of a Band-pass R-C filter. 5'
- (ii) A band-pass filter **consists** of two R-C networks connected in cascade. The low-pass filter consists of resistance $R_1 = 10\text{K}\Omega$ and capacitor $C = 100\mu\text{F}$ and high-pass filter **consists** of $R_2 = 1\text{M}\Omega$ and $C_2 = 0.01\mu\text{F}$.

Find the lower and upper cut-off frequencies and the band pass gain.

5. (a) Discuss the Foster methods of Network synthesis. 5

(b) The driving point impedance of an LC network is given by

$$Z(s) = \frac{10(s^2+4)(s^2+16)}{s(s^2+9)}$$

Obtain the Foster 1st form of network. 5

6. Write short notes on (any' two) 2x5

- (a) Bode diagram.
 (b) Characteristics impedance of a network.
 (c) Hybrid parameters of a network.
 (d) Jr to T transformation of network.