

2009**M.Sc.****2nd Semester Examination****ELECTRONICS****PAPER—EL-1202****Full Marks : 40****Time : 2 Hours**

The figures in the right-hand margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Illustrate the answers wherever necessary.

Answer Q. No. 1 and any three from the rest.

- 1. Answer any five questions : 2×5**
- (a) Prove that $A \oplus B \oplus \overline{C} = \overline{A \oplus B \oplus C}$.
 - (b) What is the major advantage and disadvantage of flash ADC ?
 - (c) Derive the characteristic equation of a D flip-flop from the characteristic equation of a JK flip-flop.
 - (d) Define the Fan-out of a logic gate.
 - (e) Which input of a commercially available decoder IC chip can be utilised to use the decoder as a demultiplexer ?
 - (f) What do you mean by Figure of Merit of a digital IC ?
 - (g) Which theorem has been utilised for developing the method of minimisation of Boolean function using K-map ?
 - (h) Write down the function of chip select and Read/Write input of a memory chip.

(Turn Over)

2. (a) How an 8-to-1 MUX can be designed using all 4-to-1 MUXs ? (No other logic can be used). Draw the circuit and explain the operation.
- (b) How a 4-to-1 MUX can be converted to a 2-to-1 MUX ? 6+4

3. Using a 4-to-16 decoder design a circuit with following feature :

"Circuit should produce logic-1 output when the 4-bit binary input to the decoder is divisible by 3 but greater than 5. 10

4. (a) Find out the minimal expression of the given function :

$$F = \sum m(3, 4, 5, 7, 9, 13, 14, 15)$$

And draw the minimal circuit using NOR gates only.

- (b) Design a full adder circuit using a single decoder with active-low outputs and NAND gates. (4+3)+3
5. (a) Give the construction of a 555 timer IC.
- (b) Explain how the timer is used as a monostable multivibrator.
- (c) Design a circuit using 555 IC to generate of 5 KHz frequency and duty cycle 60%. 3+4+3
6. (a) Describe the relative advantages of MOS circuits as compare with BJT circuits.
- (b) Draw the circuit diagram for DRAM cell and explain its read and write operation.
- (c) Construct a CMOS circuit to implement the following Boolean function :

$$F = (A + B + C) D. \quad 1+5+4$$