

M.Sc 1st Semester Examination, 2009

ELECTRONICS

(Analog Electronics)

PAPER—EL-1104

Full Marks : 50

Time : 2 hours

Answer **Q. No. 1** and any **three** questions
from the rest

The figures in the right-hand margin indicate marks

*Candidates are required to give their answers in their
own words as far as practicable*

Illustrate the answers wherever necessary

1. Answer *all* questions : 2 × 5

(a) Explain how a R-S flip-flop can be used as a
phase comparator.

(Turn Over)

- (b) How a black and white TV receiver can reproduce a monochrome telecast on its screen ?
- (c) Explain the function of a Bridge amplifier as a transducer.
- (d) What is the slew rate of an OP-AMP ? Write down its ideal value.
- (e) Draw the circuit diagram of an Instrumentation amplifier.
2. (a) Draw the block diagram of a phase locked loop and explain its principle of operation.
- (b) Discuss how a PLL circuit can be used as a frequency multiplier.
- (c) What is state variable filter ? 4 + 4 + 2
3. (a) How is synchronization between scanning at the TV transmitter and receiver is obtained ?

(b) Define the terms frame and field.

(c) Draw the schematic diagrams of a colour camera and a shadow-mask colour tube and explain their operation. 3 + 2 + 5

4. (a) Discuss with suitable diagram how a differential equation can be solved using OP-AMP circuits.

(b) Explain the operation of a square wave-generator using proper circuit diagram and derive the expression of its output frequency. 5 + 5

5. (a) Write down the differences between series and shunt regulation of voltage.


(b) Draw the circuit diagram of a voltage regulator using OP-AMP as a comparator and explain its operation. Derive also its output voltage.

(c) What do you mean by monolithic voltage regulators ? 2 + (4 + 2) + 2

6. (a) Draw the circuit diagram of a triangular wave generator and explain its operation.

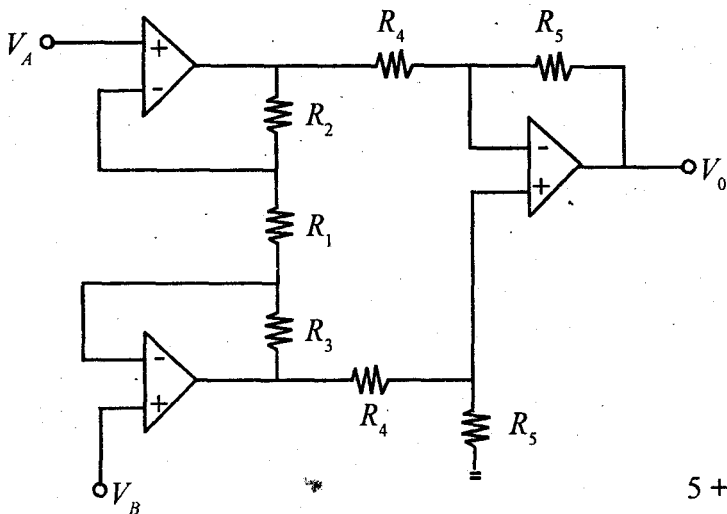(b) For the circuit of the following show that

$$V_0 = (V_B - V_A) \left(1 + 2 \cdot \frac{R_2}{R_1} \right)$$



[Internal Assessment : 10 Marks]