

M.Sc. 1st Semester Examination, 2010

ELECTRONICS

(Network Analysis & Synthesis)

PAPER—ELC- 103

Full Marks : 50

Time : 2 hours

Answer **Q.No.1** and any **three** from the rest

The figures in the right-hand margin indicate marks

Candidates are required to give their answers in their own words as far as practicable

Illustrate the answers wherever necessary

1. Answer *all* questions : 2 × 5
- (a) Write the testing procedure of positive real function.
- (b) What do you mean by characteristic impedance of a network ?

- (c) A network is expressed by following differential equation :

$$\frac{5 d^2 y}{dt^2} + \frac{3 dy}{dt} + 2y = \frac{2 dx}{dt} + x$$

where, 'X' is input and 'Y' is output obtain the transfer function.

- (d) What is Bode diagram ?

- (e) The impedance of a circuit is given by

$$\vec{Z} = 5 + j6 \Omega$$

Find the conductance of the circuit with its unit.

2. (a) The Reduced incidence matrix of a network is given below :

		Branches →					
		1	2	3	4	5	6
Nodes ↑	a	1	0	0	-1	0	-1
	b	0	1	0	1	-1	0
	c	0	0	1	0	1	1
	d						

(i) Obtain the complete incidence matrix.

(ii) Without drawing the connected graph, find the branches in series and in parallel.

(b) Using Thevenin's theorem, determine the current through $10\ \Omega$ resistance of the circuit as shown in Fig 1.

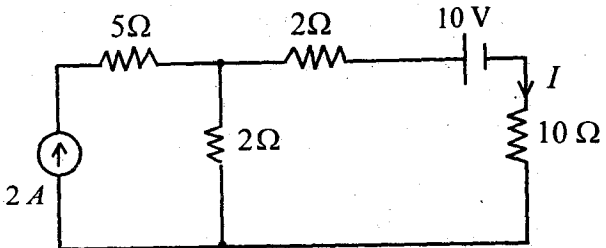


Fig. 1

$$(2 + 1\frac{1}{2} + 1\frac{1}{2}) + 5$$

3. (a) The following readings were obtained experimentally for an unknown two-port network. Determine the Y -parameters.

	I_1	I_2	V_1	V_2
Output shorted	5 mA	0.3 mA	25 V	0
Input shorted	5 mA	10 mA	0	30 V

(b) The system function of a network is given :

$$H(S) = \frac{S(S+2)}{(S+1)(S^2+4S+13)}$$

Draw Pole-zero diagram.

4. (a) For the network as shown in Fig. 2, find I , I_C in phasor form. Also draw phasor diagram
Given :

$$V(t) = 220\sqrt{2} \sin 314t$$

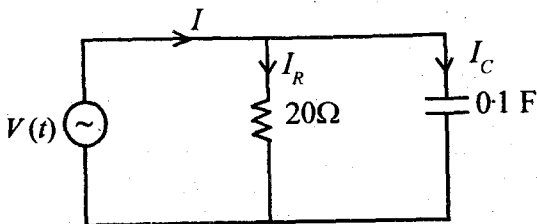


Fig. 2

- (b) State the conditions for which a system function $H(S)$ is said to be positive real function.
- (c) The system function of a network is given by

$$H(S) = \frac{S^2 + 10S + 4}{S + 2}$$

Test whether it is a positive real function or not.

5. (a) Find the 3dB bandwidth of the circuit of Fig. 3.

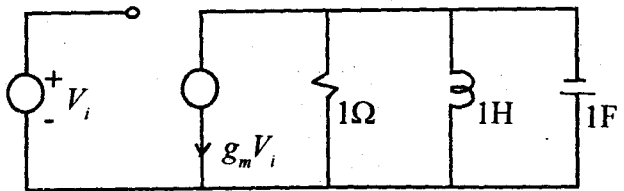


Fig. 3

- (b) Perform continued fraction expansion of

$$Y(S) = \frac{S^3 + 2S^2 + 3S + 1}{S^3 + S^2 + 2S + 1}$$

and draw the network.

5 + 5

6. (a) The driving point impedance of an LC network is given by

$$Z(S) = \frac{4S(S^2 + 4)}{(S^2 + 1)(S^2 + 16)}$$

obtain Foster form of network.

(b) The driving point impedance of a R - C network is given by

$$Z(S) = \frac{S^2 + 8S + 5}{S(S+4)}$$

obtain Caver form of network.

5 + 5

[*Internal Assessment* : 10 Marks]
