

**M.Sc. 1st Semester Examination, 2010**

**ELECTRONICS**

( *Analog Electronics* )

PAPER—ELC-104

*Full Marks : 50*

*Time : 2 hours*

Answer **Q. No. 1** and any **three** from the rest

*The figures in the right-hand margin indicate marks*

*Candidates are required to give their answers in their own words as far as practicable*

*Illustrate the answers wherever necessary*


1. Answer **all** questions : 2 x 5

(a) What is SMPS ? Write down its differences from an ordinary power supply ?

(b) Write down the advantages of active filters over passive ones.

( Turn Over )

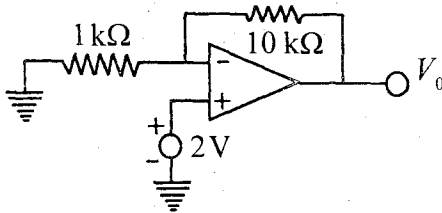- (c) Find out  $V_0$  of the following circuit.




- (d) The output of an adder having three inputs is such that it is equal to the sum of the inputs with a negative sign. Draw the necessary circuit.
- (e) Explain the term synchronization related television.
2. (a) Draw the circuit diagram of an active low pass 1st order Butterworth filter and describe its principle of operation.
- (b) Define the terms Roll Off Rate and cut-off frequency for the above filter.
- (c) Design a first order active high pass Butterworth filter at a cut-off frequency 1 kHz and a pass band gain of 2.      4 + 3 + 3

3. (a) Draw schematic diagram of a vidicon TV camera tube and describe its operation.
- (b) What do you mean by interlaced scanning? How it operates?
- (c) Explain why integrators are invariably preferred to differentiators in analog computations.  $3 + (2 + 2) + 3$
4. (a) Draw the circuit diagrams of logarithmic and antilogarithmic amplifiers using  $I_C 741$  and explain their operations.
- (b) Using logarithmic and antilogarithmic amplifiers discuss how analog multiplication and division could be performed.  $6 + (2 + 2)$
5. (a) Describe how phase detection could be achieved in PLL using XOR phase detector.

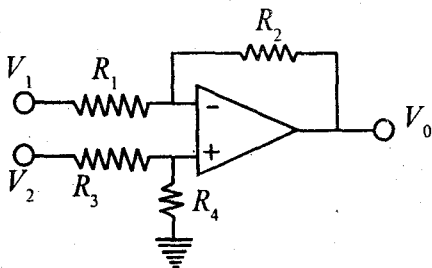- (b) What is frequency shift keying ?
- (c) Discuss the principle of operation of a Schmitt trigger.
- (d) For the following circuit prove that


$$V_0 = V_2 \left( \frac{R_1 + R_2}{R_3 + R_4} \right) \frac{R_4}{R_1} - V_1 \frac{R_2}{R_1}$$



3 + 1 + 2

6. (a) What do you mean by a voltage controlled oscillator?
- (b) Explain the principle of operation of a VCO using proper circuit diagram.

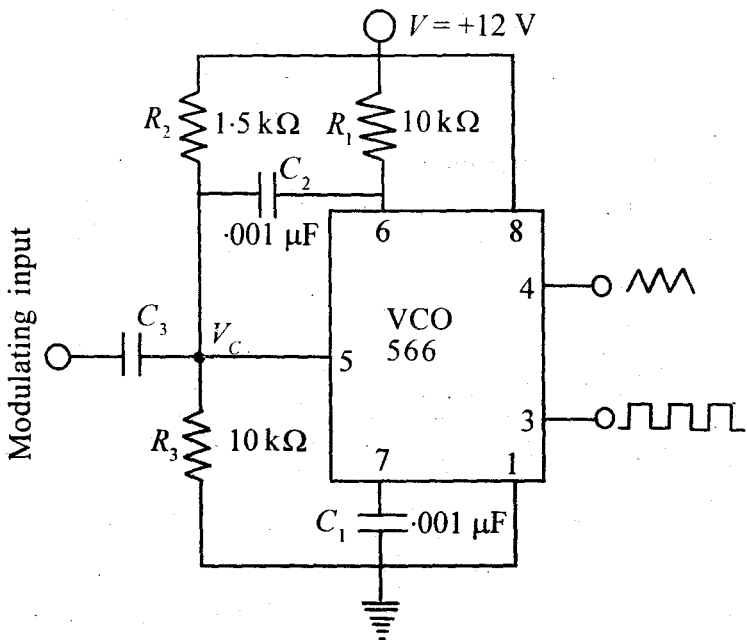- (c) The circuit with the values of the components is shown below:



- Determine the nominal frequency of the output waveforms.
- Compute the modulation in the output frequencies if  $V_C$  is varied between  $9.5\text{ V}$  and  $11.5\text{ V}$ .

(iii) Draw the square-wave output waveform if the modulating input is a sine wave.

(d) Discuss how you can generate a variable power supply using  $I_C$  LM 317. 1 + 3 + 3 + 3

[*Internal Assessment* : 10 Marks ]

