

M.Sc 1st Semester Examination, 2010

ELECTRONICS

(Electronic Circuit Laboratory)

PAPER – ELC -106

(Practical)

Full Marks : 50

Time : 3 hours

Answer any **one question, selecting it
by a lucky draw**

The figures in the right-hand margin indicate marks

(Turn Over)

1. Design a regulated power supply of variable output using LM 317.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Circuit implementation on bread board. 3
 - (d) Recording of data for load and line regulation characteristics (one set each). 5 + 5
 - (e) Drawing of graphs. 4 + 4
 - (f) Calculation of percentage regulation and stability factor for $I_L = \dots\dots$ mA and $V_{il} = \dots\dots$ V respectively. 2 + 2
 - (g) Discussion of the results obtained. 3

2. Design a regulated power supply using 78 XX group (regulator) and study its performance.
- (a) Working formula. 4
 - (b) Drawing of circuit diagram with labelling. 3
 - (c) Implementation of the circuit on a bread board. 3
 - (d) Recording of data for load and line regulation characteristics (one set each). 5 + 5
 - (e) Drawing of graphs. 4 + 4
 - (f) Calculation of percentage regulation and stability factor for $I_L = \dots\dots$ mA and $V_{il} = \dots\dots$ V respectively. 2 + 2
 - (g) Discussion of the results obtained. 3

3. Design a regulated power supply using power transistor as a pass element and another transistor as a comparator.

Output current = mA, output voltage =V.

- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design considerations. 4
- (d) Circuit implementation on a bread board. 4
- (e) Recording of data for load and line regulation characteristics.(one set each) 4 + 4
- (f) Drawing of graphs. 3 + 3
- (g) Calculation of percentage regulation and stability factor at $I_L = \dots\dots\dots$ mA, and $V_{il} = \dots\dots\dots$ V respectively. 2 + 2
- (h) Discussion about the results obtained. 2

4. Design a regulated power supply using a power transistor as a pass element and an OPAMP as comparator.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations. 4
 - (d) Circuit implementation on a bread board. 4
 - (e) Recording of data for load and line regulation characteristics. (one set each). 4 + 4
 - (f) Drawing of graphs. 3 + 3
 - (g) Calculation of percentage regulation and stability factor at $I_L = \dots\dots$ mA and $V_{il} = \dots\dots$ V respectively. 2 + 2
 - (h) Discussion about the results obtained. 2

5. Study the performance of a logarithmic amplifier using OPAMP.
- (a) Working formula. 4
 - (b) Drawing of circuit diagram with labelling. 3
 - (c) Implementation of the circuit on a bread board. 3
 - (d) Recording of data by varying the input voltage from 0 to 3 V at steps of 0.1 V. 10
 - (e) Drawing of characteristic curves . 4 + 4
 - (f) Discussion about the nature of curves and the results obtained. 3
 - (g) Writing of possible applications of the circuit using the results obtained. 4

6. Study the performance of an antilogarithmic amplifier using OPAMP.
- (a) Working formula. 4
 - (b) Drawing of circuit diagram with labelling. 3
 - (c) Implementation of the circuit on a bread board. 3
 - (d) Recording of data by varying the input voltage. 10
 - (e) Drawing of characteristic curves. 4 + 4
 - (f) Discussion about the curves and the results obtained. 3
 - (g) Discussion of possible applications of the circuit using the results obtained. 4

7. Design a first order low-pass active Butterworth filter and study its performance.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations for cut-off frequency =Hz and gain = 5
 - (d) Implementation of the circuit on a bread board. 3
 - (e) Recording of data for frequency response characteristics. 8
 - (f) Drawing of graph. 4
 - (g) Finding the cut-off-frequency and comparison of it with the supplied value. 2 + 2
 - (h) Finding the Roll-off-rate for the filter. 2
 - (i) Discussion of the results obtained. 2

8. Design a first order active high-pass Butterworth filter and study its performance.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations for cut-off frequency =Hz and gain = 5
 - (d) Implementation of the circuit on a bread board. 3
 - (e) Recording of data for frequency response characteristics. 8
 - (f) Drawing of graph. 4
 - (g) Finding the cut-off-frequency and comparison of it with the supplied value. 2 + 2
 - (h) Finding the Roll-off-rate for the filter. 2
 - (i) Discussion of the results obtained. 2

9. Design a second order active low-pass Butterworth filter and study its performance.
- (a) Working formula. 4
 - (b) Circuit diagram with labelling. 3
 - (c) Design considerations for cut-off frequency =Hz and gain = 5
 - (d) Implementation of the circuit on a bread board. 3
 - (e) Recording of data for frequency response characteristics and drawing graph. 8 + 4
 - (f) Finding the cut-off-frequency and comparison of it with the supplied value. 2 + 2
 - (g) Finding the Roll-off-rate for the filter. 2
 - (h) Discussion of the result obtained. 2

10. Design a second order active high-pass Butterworth filter and study its performance.

- (a) Working formula. 4
- (b) Circuit diagram with labelling. 3
- (c) Design considerations for cut-off frequency =Hz and gain = 5
- (d) Implementation of the circuit on a bread board. 3
- (e) Recording of data for frequency response characteristics and drawing graph. 8 + 4
- (f) Finding the cut-off-frequency and comparison of it with the supplied value. 2 + 2
- (g) Finding the Roll-off-rate for the filter. 2
- (h) Discussion about the results obtained. 2

Distribution of Marks

Experiment	– 35
Viva voce	– 10
L.N.B	– 05
<u>Total</u>	<u>– 50</u>

